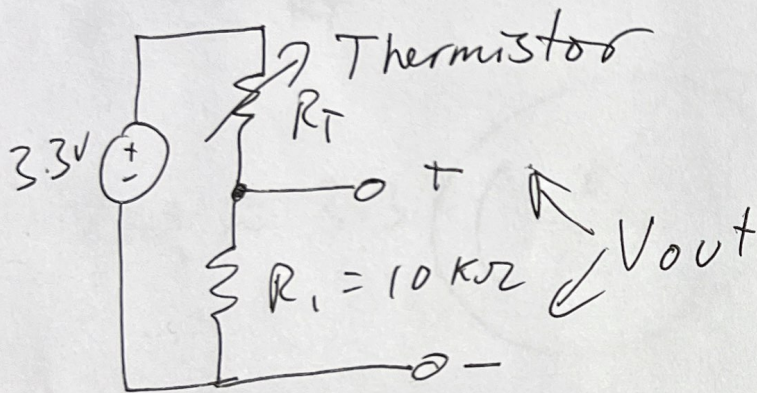


Temperature controlled R

①

$$R = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{T_0} \right)}$$

$$R(T_0) = R_0 e^{\beta \left(\frac{1}{T_0} - \frac{1}{T_0} \right)} = R_0 e^{0} = R_0$$



$$\textcircled{1} \quad V_{out}(R_T) = 3.3 - V_{R_1} - V_{R_T}$$

$$I_{R_1}$$

$$V_{R_1} = I R_1 ; V_{R_T} = I R_T$$

$$I = \frac{3.3}{R_1 + R_T}$$

$$\textcircled{2} \quad V_{out}(R_T) = 3.3 - \frac{3.3 R_1}{R_1 + R_T} - \frac{3.3 R_T}{R_1 + R_T}$$

$$= 3.3 \left(1 - \frac{R_1}{R_1 + R_T} - \frac{R_T}{R_1 + R_T} \right)$$

$$= 3.3 \left(1 - \left(\frac{R_1 + R_T}{R_1 + R_T} \right) \right)$$

$$V_{out} = 3.3 \left(1 - \frac{R_T}{R_1 + R_T} \right) = 3.3 \left(\frac{R_1 + R_T - R_T}{R_1 + R_T} \right)$$



$$V_{out} = 3.3 \left(\frac{R_1}{R_1 + R_T} \right)$$

$$\Delta T \rightarrow \Delta V_{out}$$

$$R_1 \gg R_T$$

$$R_1 \ll R_T$$
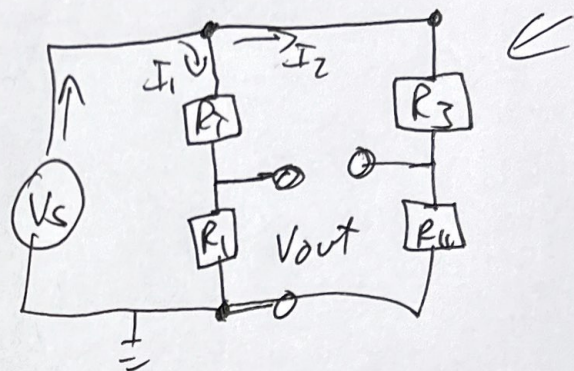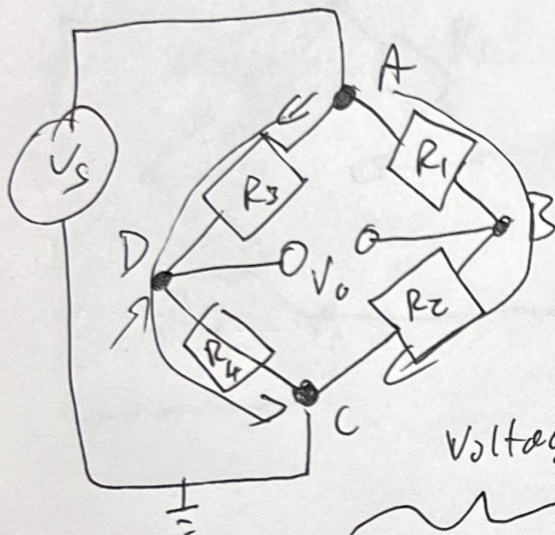
$$V_{out} \approx 3.3 \left(\frac{R_1}{R_T} \right)$$




Voltage @ D: V_D


$$V_o = (V_s - V_{AD}) - (V_s - V_{AB})$$

$$= V_s \left(\frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$
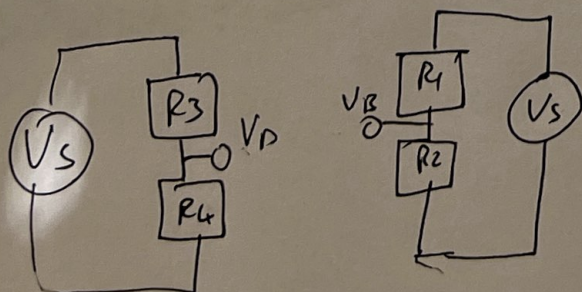
$$= V_s \frac{(R_1 R_4 - R_2 R_3)}{(R_1 + R_2)(R_3 + R_4)} = \frac{(R_1 + \Delta R_1) R_2 - R_2 R_3}{(R_1 + \Delta R_1 + R_2)(R_3 + R_4)}$$



$$= V_s \frac{\Delta R_1}{4R}$$

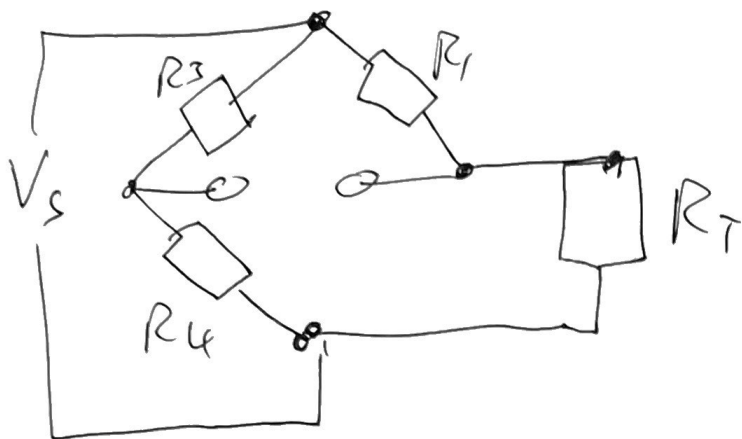


$$V_{out} \approx V_s \frac{\Delta R_T}{4R}$$



Sensitivity

$$\frac{\Delta V_{out}}{\Delta T} \quad (\text{Temperature sensor})$$

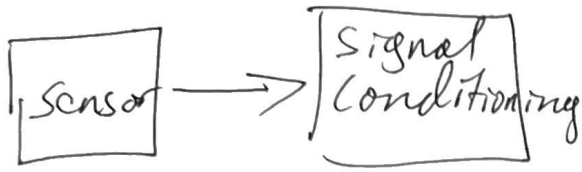
$$\frac{\Delta \text{Current}}{\Delta \text{Optical Power}} \quad (\text{Light})$$



Op Amp

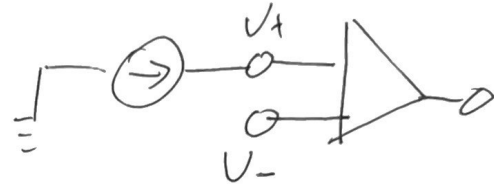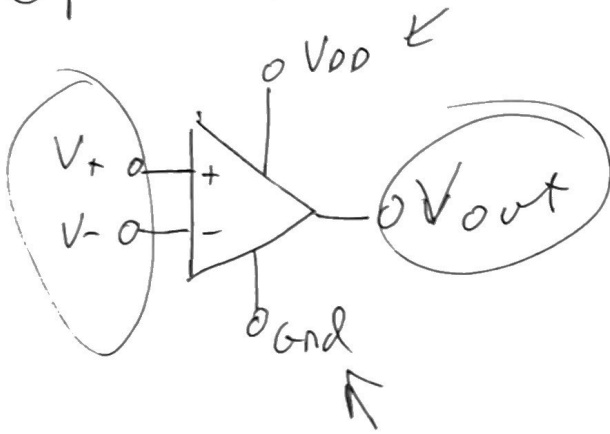

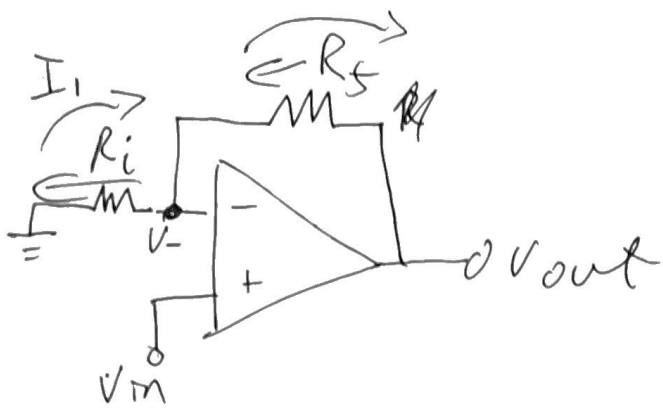- ① There is NO current that flows into the inputs V^+ , V^-
- ② The voltage of the two inputs is always the same
- ③ The output can support whatever current is needed



$R_i = R$ input
 $R_f = R$ feedback

$$V_{out} = ? = V_{in} + V_{R_f}$$


$$I_1 = \frac{V_-}{R_i} = \frac{V_{in}}{R_i}$$

$$V_{R_f} = I_1 R_f$$

$$V_{out} = V_{in} - \frac{I_1 R_f}{R_f} = V_{in} + \left(\frac{V_{in}}{R_i} \right) R_f = V_{in} \left(1 + \frac{R_f}{R_i} \right)$$

$$= V_{in} \left(\frac{R_i + R_f}{R_i} \right)$$


Inverting Op Amp

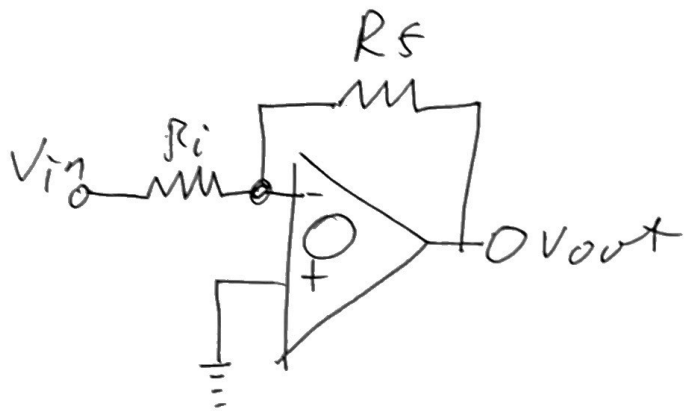

$$\frac{V_{in} - 0}{R_i} = \frac{0 - V_{out}}{R_f}$$

$$\frac{V_{in}}{R_i} = \frac{-V_{out}}{R_f}$$

$$V_{out} = -V_{in} \frac{R_f}{R_i}$$

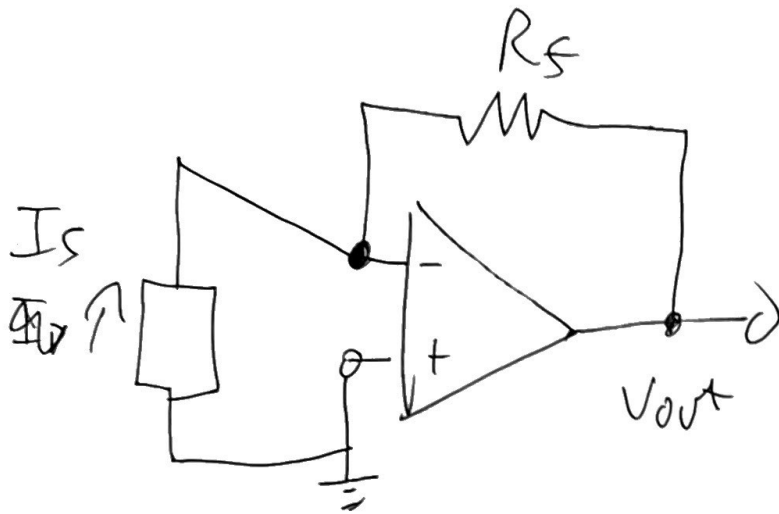

$$\frac{0 - V_{out}}{R_f} = I_s$$

$$\frac{-V_{out}}{R_f} = I_s$$

$$V_{out} = -I_s R_f$$