


m

①

- ① Current, Voltage
- ② Voltage sources
- ③ Resistors
- ④ Kirchhoff's Current Law (KCL)
- ⑤ Kirchhoff's Voltage Law (KVL)

① Current

- flow of chg across some region
- Positive flow charge flow

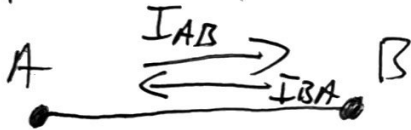

Case 1: $\begin{matrix} + \rightarrow \\ + \rightarrow \end{matrix}$

$$I_{AB} > 0 ; I_{BA} < 0$$

Case 2: $\begin{matrix} \rightarrow \\ \rightarrow \end{matrix}$


$$I_{AB} < 0 ; I_{BA} > 0$$

② Voltage


- Relative "force" or "pressure" charges moving between 2 points feel
- Voltage is always defined ~~in a~~ relatively

② Voltage sources

②

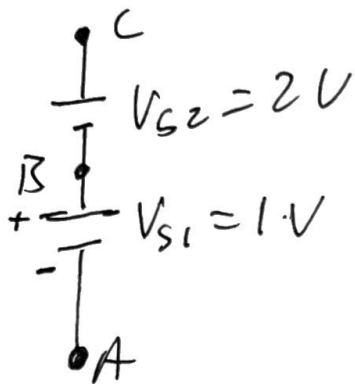

→

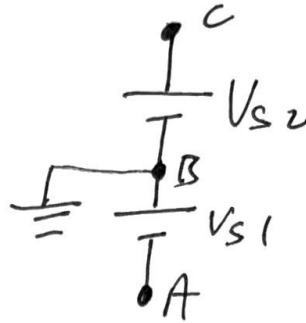

$$V_A = -1V$$

$$V_B = 0$$

$$V_C = 2V$$

$$V_{AB} = V_A - V_B = -1V$$


$$V_{BA} = V_B - V_A = 1V$$

$$V_{CB} = V_C - V_B = 2V$$

$$V_{BC} = -V_{CB} = -2V$$

$$V_{CA} = V_C - V_A = 3V$$

$$2V - (-1V) = 3V$$

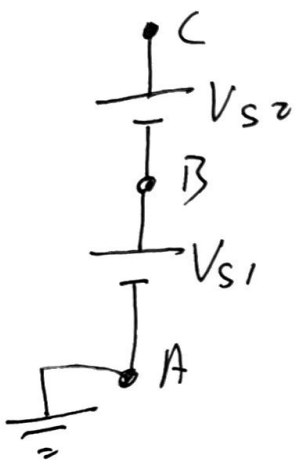

$$V_A = 0$$

$$V_B = 1$$

$$V_C = 3$$

$$V_{BA} = 1V$$



$$V_{CB} = 2V$$

$$V_{CA} = 3V$$

③ Resistors

$$V = IR$$

Series R

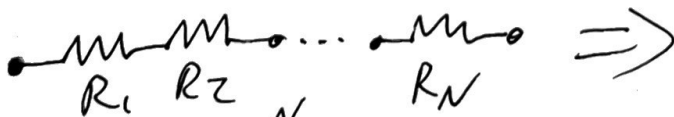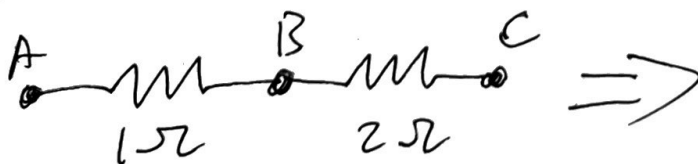


$$R_{Eq} = \sum_{i=1}^N R_i$$

③ Resistors


③

Parallel R_s

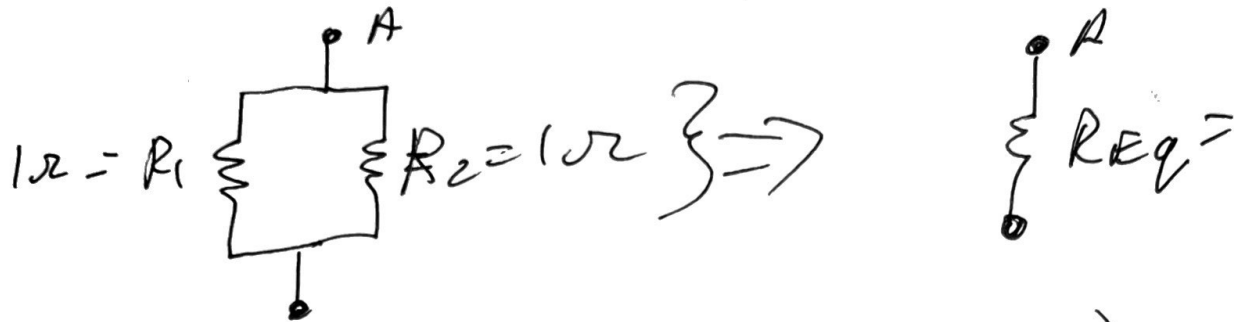

$$\left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{1}{R_{Eq}} = \left(\frac{1}{1} + \frac{1}{1} \right) = 2$$


$$R_{Eq} = \frac{1}{2} \Omega$$

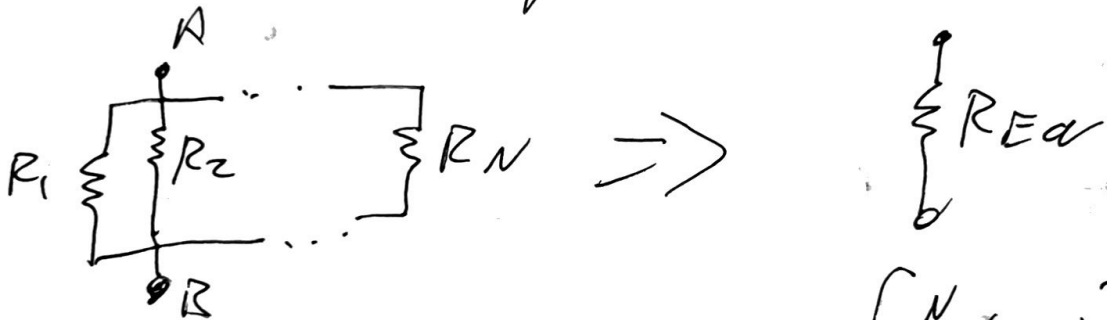

$$\sum_{i=1}^N \frac{1}{R_i} = \frac{1}{R_{Eq}} ; \quad R_{Eq} = \left[\sum_{i=1}^N \left(\frac{1}{R_i} \right) \right]^{-1}$$


④ Kirchhoff's Current Law

④

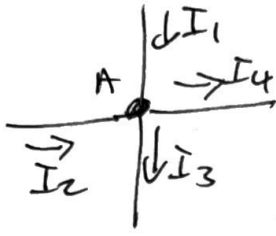

Currents in: $I_1 + I_2 =$ Currents out: $I_3 + I_4$

$$I_1 + I_2 = I_3 + I_4$$

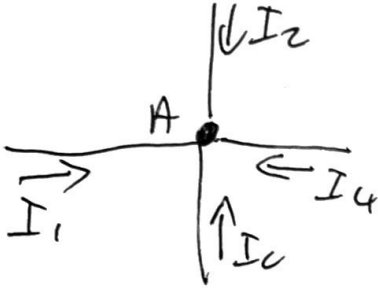


Currents in: $I_1 + I_2 + I_3 + I_4 = 0$

Currents out: $0 +$


$$I_1 + I_2 + I_3 + I_4 = 0$$

⑤ Kirchhoff's Voltage Law?

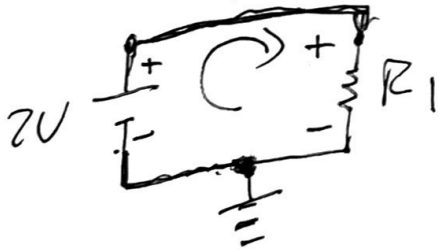

$$-2V + V_{R1} = 0$$

$$V_{R1} = 2V$$

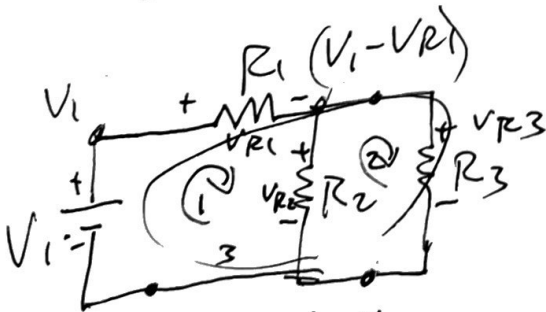

Loop 1:


$$-V_1 + V_{R1} + V_{R2} = 0$$

Loop 3:

$$-V_1 + V_{R1} + V_{R3} = 0$$

Loop 2:

$$-V_{R2} + V_{R3} = 0$$

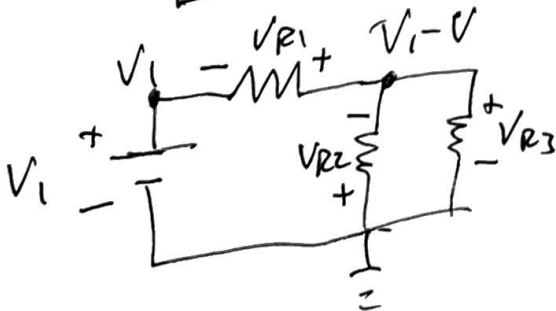

Loop 2

⑤

$$V_{R2} = V_{R3}$$

Loop 1

$$-V_1 + V_{R1} + V_{R2} = 0$$

$$V_{R1} + V_{R2} = V_1$$


$$-V_1 +$$

$$V_{R1} + V_{R3} = V_1$$

$$V_1 - V_{R1} = V_{R2}$$

$$V_1 - V_{R1} = V_{R3}$$

⑤ Kirchhoff's Current Law

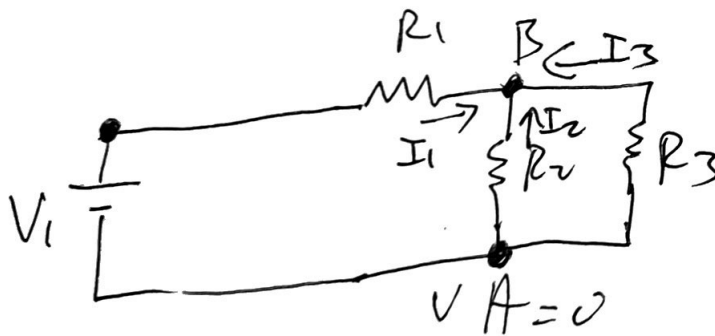

Current in	Current at
$I_1 + I_2 + I_3 =$	0
Node B \uparrow	

$$-I_1 - I_2 - I_3 = 0$$

$$-I(I_1 + I_2 + I_3) = 0$$


$$I_1 = \frac{V_{R1}}{R_1} = \frac{V_1 - V_B}{R_1}$$

$$I_3 = \frac{V_A - V_B}{R_3}$$

$$I_2 = \frac{V_A - V_B}{R_2}$$

⑥

Resistor

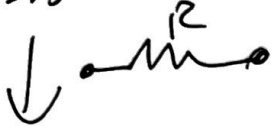

$$V_R = I_R R$$

Inductor



$$V = L \frac{di}{dt}$$

Capacitor

$$I = C \frac{dv}{dt}$$