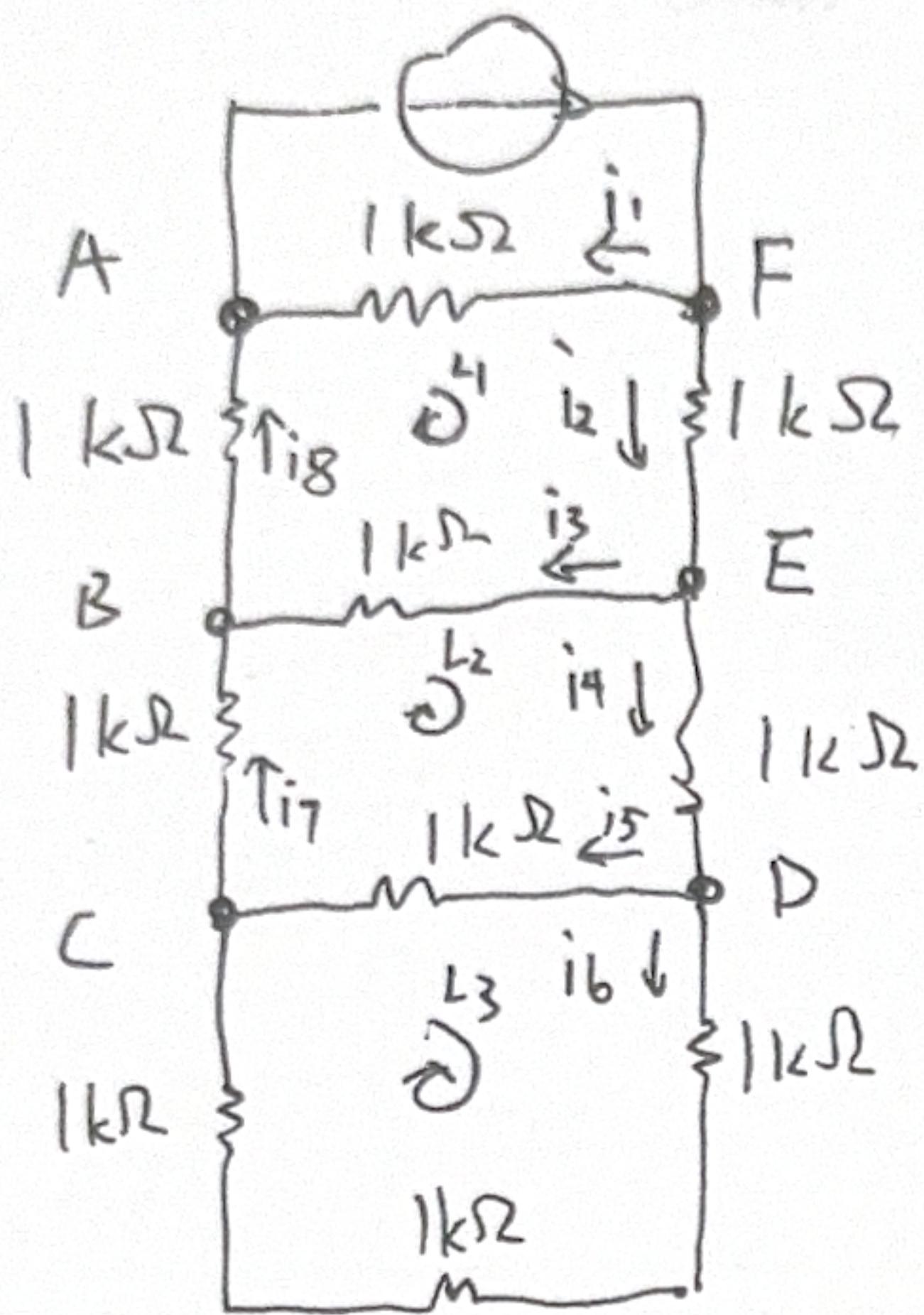


1.



(a) Equivalent resistance

$$R_{eq} = \frac{1}{\frac{1}{1000} + \frac{1}{2000} + \frac{1}{3000} + \frac{1}{2000} + \frac{1}{1000} + \frac{1}{5000}}$$

$$= \frac{41}{56} \times 1000 \Omega \approx 732 \Omega$$

(b) There are 6 nodes, denoted as A, B, C, D, E, F

There are 3 Loops - denoted as

L_1, L_2, L_3

(FEB) (EDCB) (D, C)

$$KCL: IA = i_1 + i_2$$

$$KVL: L_1 \quad i_1 \cdot 1k\Omega = i_2 \cdot 1k\Omega + i_3 \cdot 1k\Omega + i_8 \cdot 1k\Omega$$

$$E \quad i_2 = i_3 + i_4$$

$$L_2 \quad i_3 \cdot 1k\Omega = i_4 \cdot 1k\Omega + i_5 \cdot 1k\Omega + i_7 \cdot 1k\Omega$$

$$D \quad i_4 = i_5 + i_6$$

$$L_3 \quad i_5 \cdot 1k\Omega = i_6 \cdot 3k\Omega$$

$$C \quad i_7 = i_5 + i_6$$

$$B \quad i_8 = i_3 + i_7$$

$$A \bullet IA = i_1 + i_8$$

(1) Solve previous KCL and KVL, we have

$$i_1 = 0.732 \text{ A}$$

$$i_2 = i_8 = 0.268 \text{ A}$$

$$i_3 = 0.196 \text{ A}$$



$$i_4 = i_7 = 0.0714 \text{ A}$$

$$i_5 = 0.0536 \text{ A}$$


$$i_6 = 0.0179 \text{ A}$$

Voltages are

shown below

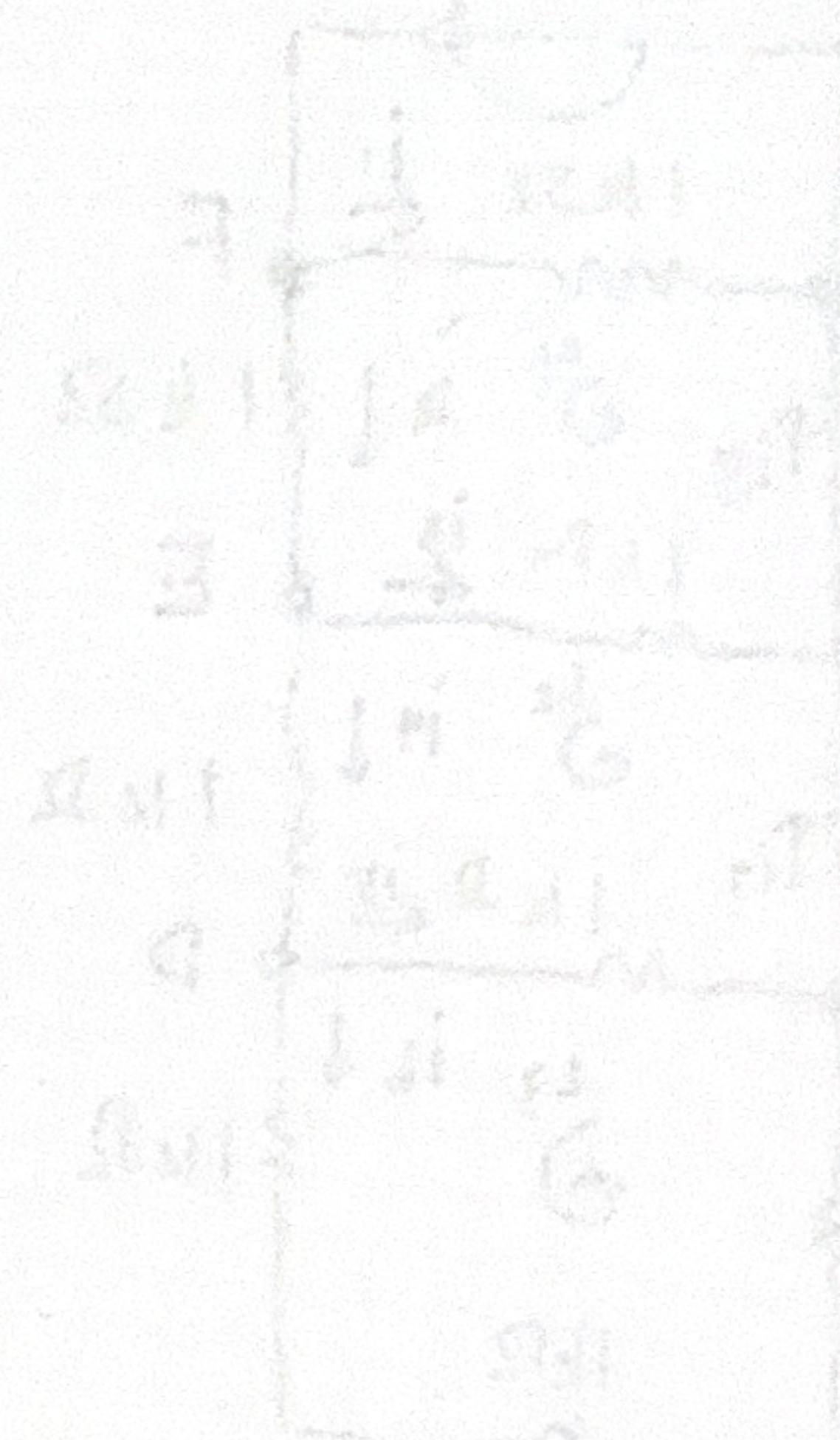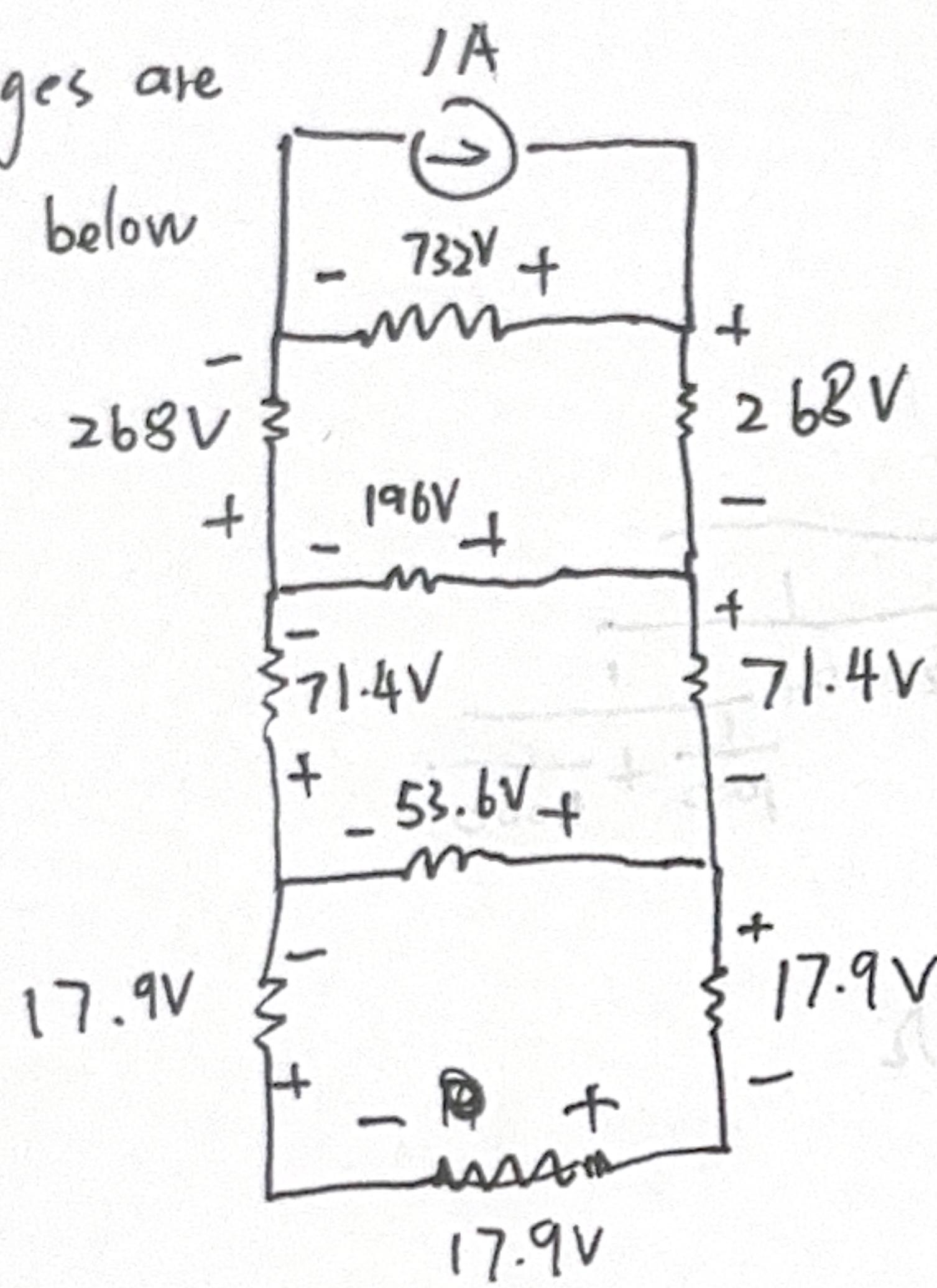

2.

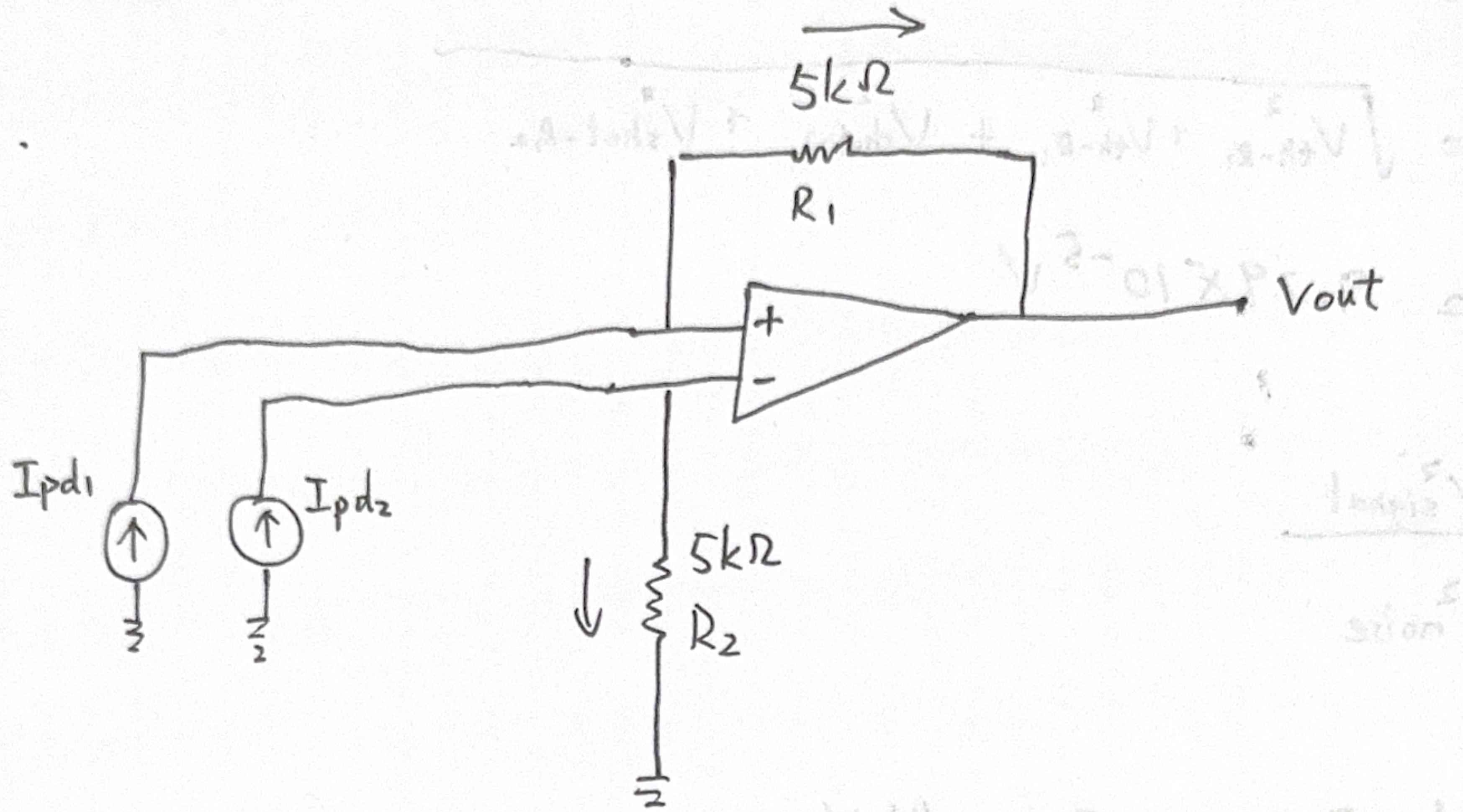

$$(a) V^+ = V^-$$

$$V_{out} + I_{pd1} \cdot 5k\Omega = 0V + I_{pd2} \cdot 5k\Omega$$

$$I_{R1} = I_{pd1}$$

$$V_{out} = (I_{pd2} - I_{pd1}) \cdot 5k\Omega$$

$$I_{R2} = I_{pd2}$$

$$(b) \text{ Resistor thermal voltage} \quad k_B = 1.38 \times 10^{-23} \text{ J/K}$$

$$V_{noise} = \sqrt{4 k_B T R \Delta f} = 2.88 \times 10^{-6} \text{ V} \quad \text{on } R_1 \text{ & } R_2 \text{ respectively}$$

PD shot noise

$$q_e = 1.60 \times 10^{-19} \text{ C}$$

$$I_{pd1\text{-noise}} = \sqrt{2 q_e I_{pd1} \Delta f}$$

$$= 1.79 \times 10^{-8} \text{ A}$$

$$I_{pd2\text{-noise}} = 5.66 \times 10^{-9} \text{ A}$$

Effective on R_1 and R_2

$$V_{shot\text{-noise}-R_1} = I_{pd1\text{-noise}} \times 5k\Omega = 8.94 \times 10^{-5} \text{ V}$$

$$V_{shot\text{-noise}-R_2} = I_{pd2\text{-noise}} \times 5k\Omega = 2.83 \times 10^{-5} \text{ V}$$

$$(c) V_{\text{noise-total}} = \sqrt{V_{\text{th-R}_1}^2 + V_{\text{th-R}_1}^2 + V_{\text{shot-R}_1}^2 + V_{\text{shot-R}_{12}}^2}$$

$$= 9.39 \times 10^{-5} \text{ V}$$

$$(d) \text{SNR} = \frac{V_{\text{signal}}^2}{V_{\text{noise}}^2}$$

$$V_{\text{out}} = (I_{\text{pd2}} - I_{\text{pd1}}) \times 5k\Omega = -45 \text{ V}$$

$$\text{SNR} = \frac{(-45 \text{ V})^2}{(9.39 \times 10^{-5}) \text{ V}^2} = 2.30 \times 10^{11}$$

Alternatively

$$\text{SIVR} = 20 \cdot (\log_{10}(V_{\text{out}}) - \log_{10}(V_{\text{noise}})) = 113.6 \text{ dB}$$

$$Q_3: I = I_0 \left(e^{\frac{qV}{nKT}} - 1 \right) \Rightarrow$$


$$I_{\min} \Rightarrow e^{\frac{qV}{nKT}} = 1 \Rightarrow \frac{qV}{nKT} = \ln(1) = 0 \Rightarrow V = 0$$

$$I_{\max} = 10 \times 10^{-3} = 1 \times 10^{-2} \times e^{\frac{qV}{nKT}} \Rightarrow$$

$$e^{\frac{qV}{nKT}} = 10^{19} \Rightarrow \frac{qV}{nKT} = 19 \ln(10) = 43.74$$

$$\Rightarrow V = 2 \times 1.38 \times 10^{-23} \times 300 \times 43.74 \times \frac{1}{1.6 \times 10^{-19}} =$$
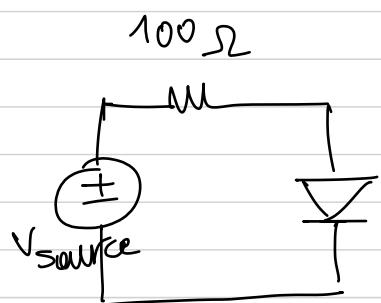
$$V_{LED} = 2.26 \times 10^4 \times 10^{-23} \times 10^{19} = 2.26 \text{ V}$$



$$V_{source} = V_R + V_{LED} \Rightarrow$$

$$V_R = R \times I = 100 \times 10 \times 10^{-3} = 1 \text{ V}$$

$$V_{source} = 1 + 2.26 = 3.26$$

max

$$V_{source \min} = 0$$

$$b) \text{ Photon Energy: } E_s = \frac{hc}{\lambda} = \frac{6.62 \times 10^{-34} \times 3 \times 10^8}{532 \times 10^{-9}} = 3.73 \times 10^{-19} \text{ J}$$

$$\text{electrons per second: } I = nq \Rightarrow n = \frac{10 \times 10^{-3}}{1.6 \times 10^{-19}} = 6.25 \times 10^{16} \text{ electrons/s}$$

$$\text{photons per second: } n_{\text{photon}} = n \times n_{\text{electron}} = 0.215 \times 6.25 \times 10^{16}$$


$$= 1.34 \times 10^{16} \frac{\text{photons}}{\text{s}}$$

$$\text{optical power} \Rightarrow P = n_{\text{photon}} \times E = 1.34 \times 10^{16} \times 3.73 \times 10^{-19} = 5.012 \text{ mW}$$

I photodiode = $R_\lambda \times P_{\text{optical}}$ based on the curve $R_\lambda \approx 0.3 \frac{\text{A}}{\text{mW}}$

$$I_{\text{ph}} = 0.3 \times 5.012 \times 10^{-3} = 0.0015 = 1.5 \text{ mA}$$

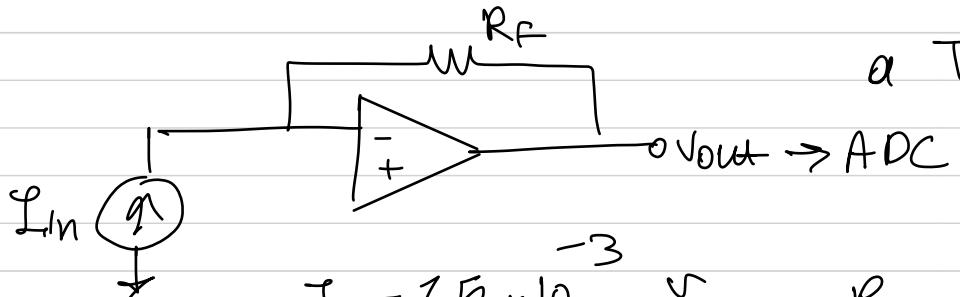Now we need to convert this current to 10 V using



$$I = 1.5 \times 10^{-3} \Rightarrow \frac{V}{R} \Rightarrow R = \frac{10}{1.5 \times 10^{-3}} \Rightarrow 6.6 \text{ k}\Omega$$

We need $R_F = 6.6 \text{ k}\Omega$ but we want to design our circuit using 100Ω resistors so we need 66, 100Ω resistors in series.

Q4:



$$500 \times 128 = 64000$$

$$\begin{array}{l} 128 \times 64 = 8192 \\ 64 \times 32 = 2048 \end{array}$$

sum
=> 74560 MAC operation

$$32 \times 10 = 320$$
$$\text{FLOPS} = 74560 \times 2 = 149120$$

b) accuracy

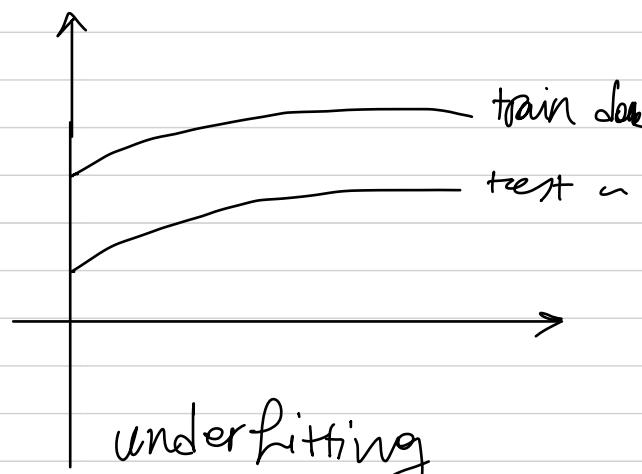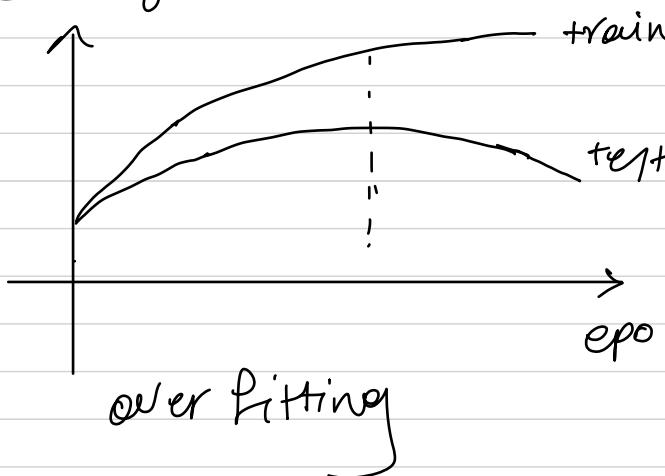

c) The rule is:

$$Y = f(x_1w_1 + x_2w_2 + \dots + \text{bias}) \quad \text{or} \quad \sum_{i=1}^n x_i w_i + b$$

f is a step function or an activation function

d) Perceptrons can only solve linearly separable


problems, they cannot handle non linearly separable datasets.

They use Step Function as activation function so

which prevents them from using gradient based method



Q 5 8

a) NAND Gate

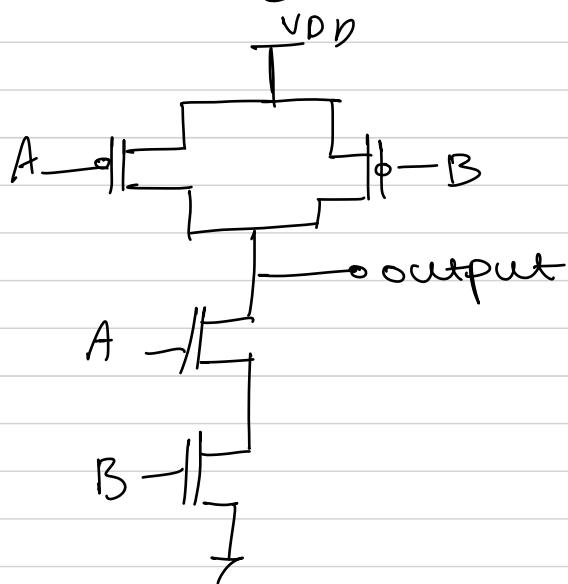


b)



A	B
0	0

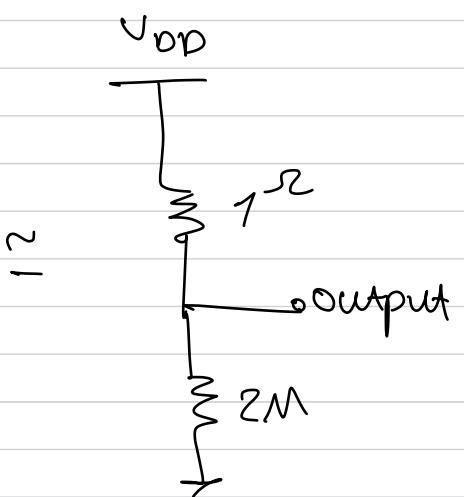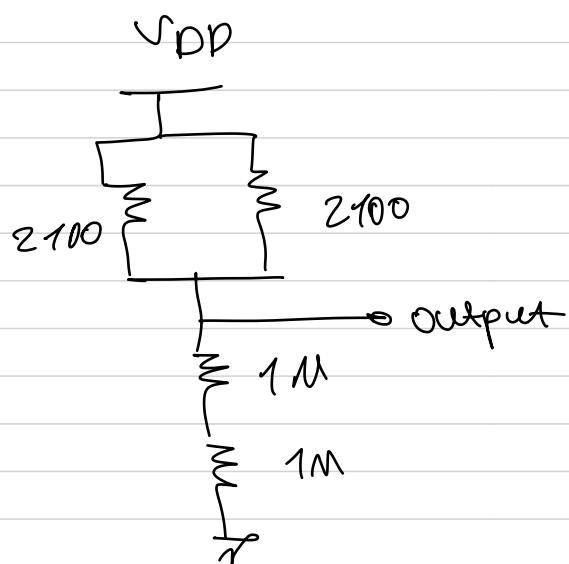
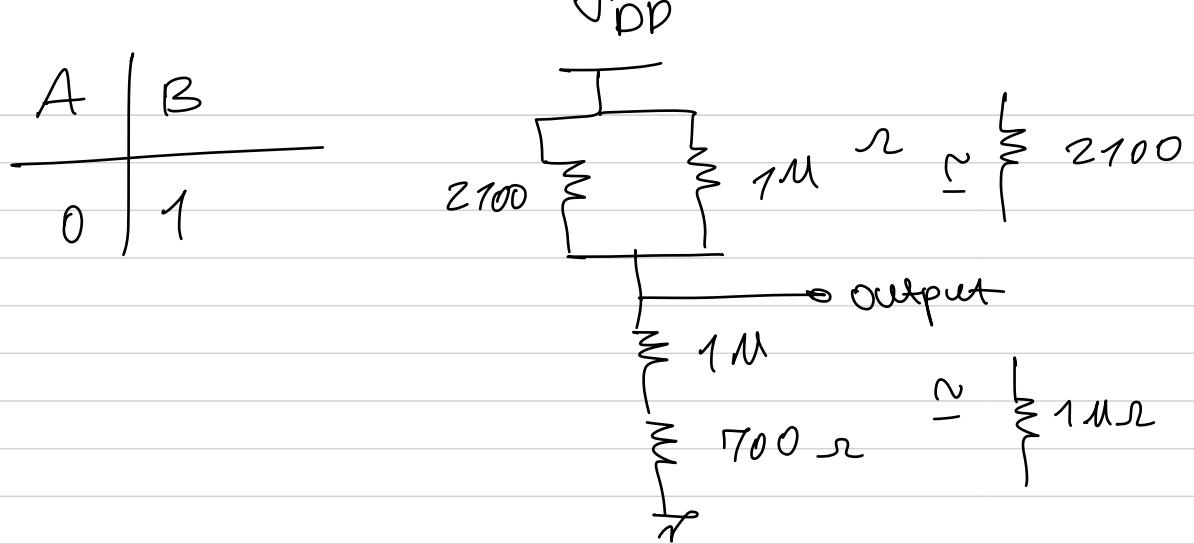
$$\text{output} \leq \frac{2 \times 2^M}{2^M} \leq 2^5$$


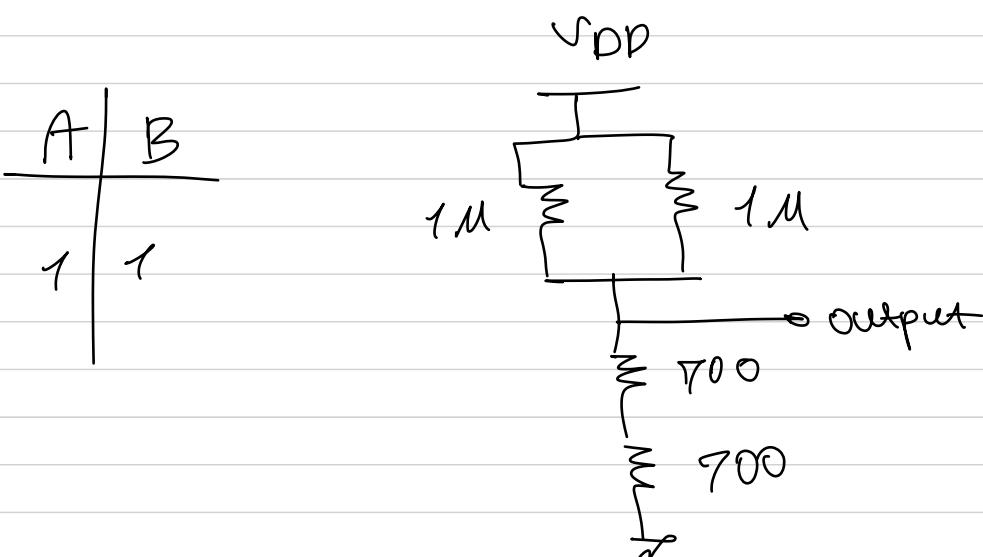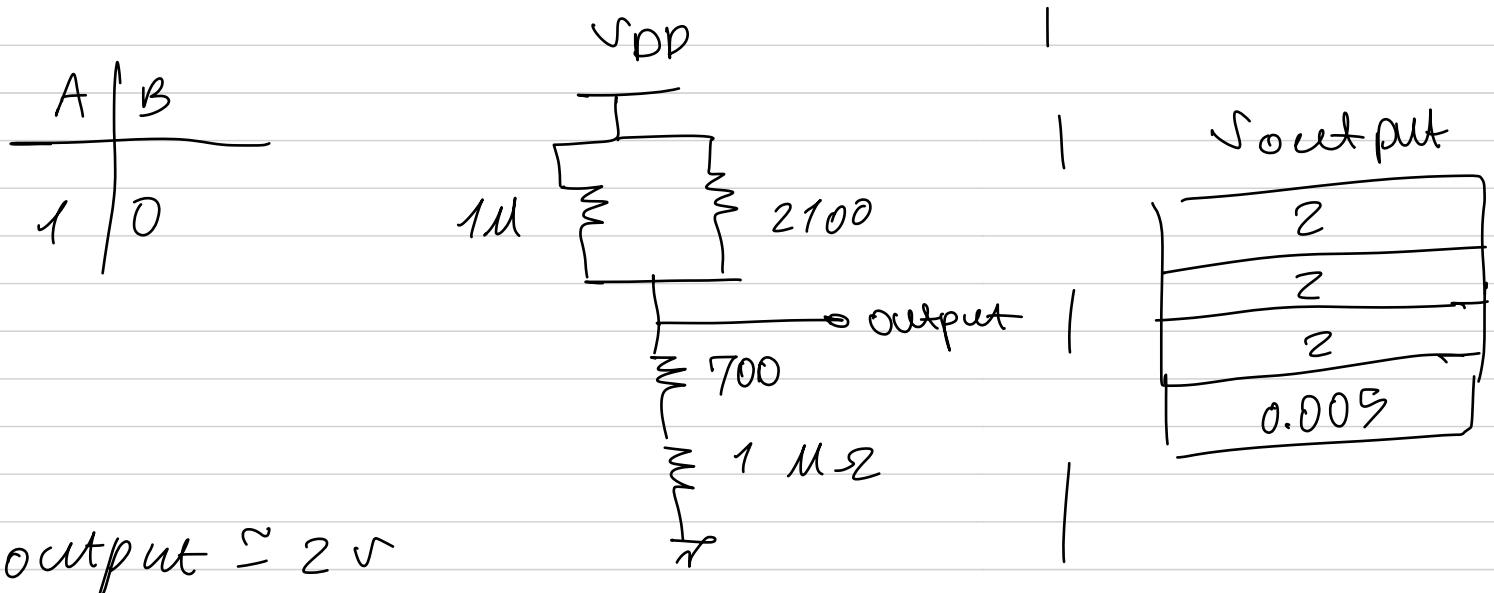
$$\text{output} \approx 2 \times \frac{1M}{1M + 700} \approx 2$$



$$\text{Output} \approx 2 \times \frac{1400}{0.5 \times 10^6} = 5600 \times 10^{-6} = 0.005$$