



• Midterm solution:

$$1. a) 15 \parallel 5 = \frac{15 \times 5}{20} = \frac{15}{4} + 10 = \frac{55}{4} \parallel 5 = \frac{\frac{55}{4} \times 5}{\frac{55}{4} + 5} =$$

$$\frac{\frac{55}{4} \times 5}{\frac{75}{4}} = \frac{55 \times 5}{75} = \frac{55}{15} = \frac{11}{3} + 10 = \frac{41}{3} \parallel 5$$

$$\frac{\frac{41}{3} \times 5}{\frac{41}{3} + 5} = \frac{41 \times 5}{96} = 3.6 \text{ k}\Omega$$

$$\left. \begin{array}{l} N_1: I_{\text{total}} = I_6 + I_7 \\ N_2: I_1 = I_5 + I_2 \\ N_3: I_2 = I_4 + I_3 \\ N_4: I_4 + I_3 + I_7 = 0 \\ N_5: I_5 + I_8 = I_7 \\ N_6: I_6 = I_{\text{total}} + I_8 \end{array} \right\} \text{KCL}$$


$$L_1: 5 = 5I_6 \Rightarrow I_6 = 1 \text{ mA}$$

$$L_2: 5I_1 + 5I_5 - 5I_8 - 5I_6 = 0 \Rightarrow I_1 + I_5 - I_8 = 1$$

$$L_3: 5I_2 + 5I_4 - 5I_7 - 5I_5 = 0 \Rightarrow I_2 + I_4 = I_7 + I_5$$

$$L_4: 15I_3 = 5I_4 \Rightarrow 5I_3 = I_4$$

c) $R_{total} = 3.6 \text{ k}\Omega$

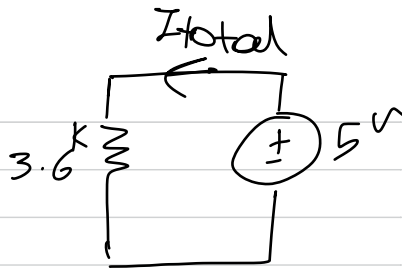

$I_{total} = 1.39 \text{ mA}$


$V_{N6} = 0 \Rightarrow V_{N1} = 5 \text{ V}$

$I_6 = 1 \text{ mA} \Rightarrow V_{N1} = 5 \text{ k}\Omega \times 1 \text{ mA} = 5 \text{ V}$

$5 = (I_1 + I_5 - I_8) \times 5 \Rightarrow I_1 + I_5 - I_8 = 1$

$I_{total} = I_6 + I_1 \Rightarrow I_1 = 1.39 - 1 = 0.39 \text{ mA} = I_1$

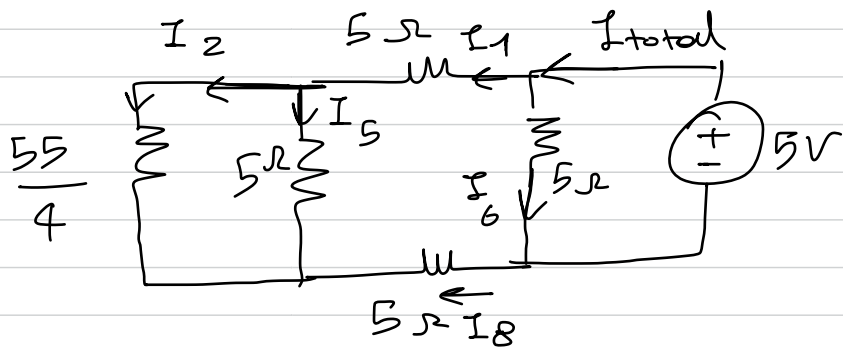$V_{N1} - V_{N2} = 5 \times 0.39 = 1.95 \Rightarrow V_{N2} = 5 - 1.95 = 3.05 \text{ V} = V_{N2}$



$I_2 = I_1 \times \frac{5 \Omega}{5 + \frac{55}{4}} = 0.104 = I_2$


$I_1 = I_2 + I_5 \Rightarrow I_5 = 0.39 - 0.104 = 0.286 = I_5$

$I_2' + I_5 + I_8 = 0 \Rightarrow I_8 = -0.39$

$5 \times I_5 = V_{N2} - V_{N5} \Rightarrow 1.43 = 3.05 - V_{N5} \Rightarrow V_{N5} = 1.62 \text{ V}$

$$I_5 + I_8 = I_7 \Rightarrow$$
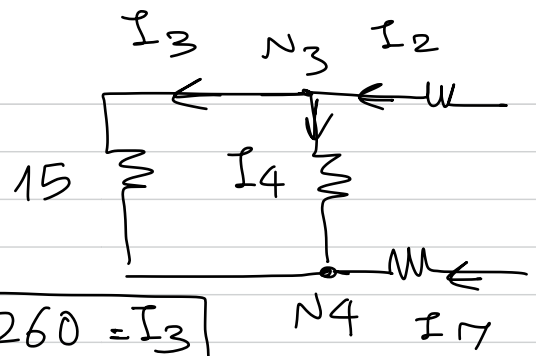
$$0.286 - 0.39 \Rightarrow \boxed{I_7 = -0.104}$$



$$I_3 = I_2 \times \frac{5}{5+15} = 0.104 \times \frac{1}{4} = \boxed{0.0260 = I_3}$$

$$I_2 = I_3 + I_4 \Rightarrow I_4 = 0.104 - 0.026 = \boxed{0.0780 = I_4}$$

$$V_{N2} - V_{N3} = 5I_2 \Rightarrow 3.05 - 5 \times 0.104 = \boxed{2.53 = V_{N3}}$$

$$V_{N3} - V_{N4} = 5I_4 \Rightarrow 2.53 - V_{N4} = \boxed{2.14 = V_{N4}}$$

$$V_{N1} = 5V$$

$$V_{N2} = 3.05$$

$$V_{N3} = 2.53$$

$$V_{N4} = 2.14$$

$$V_{N5} = 1.62$$

$$V_{N6} = 0$$

$$I_{total} = 1.39mA$$

$$I_1 = 0.39mA$$

$$I_2 = 0.104$$

$$I_3 = 0.0260$$

$$I_4 = 0.078$$


$$I_5 = 0.286$$

$$I_6 = 1mA$$

$$I_7 = -0.104$$

$$I_8 = -0.39$$

Q2:

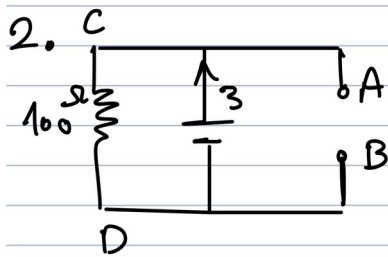


$$V_{AB} = 3V$$

$$I_{AB} = 0$$


$$I_{CD} = ? \Rightarrow V_{CD} = R_{CD} I_{CD} \Rightarrow$$

$$I_{CD} = \frac{V_{CD}}{R_{CD}} = \frac{3V}{100} = 0.03A$$

Q3:

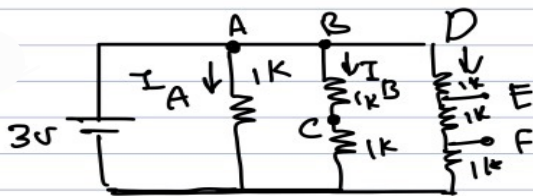

simplify

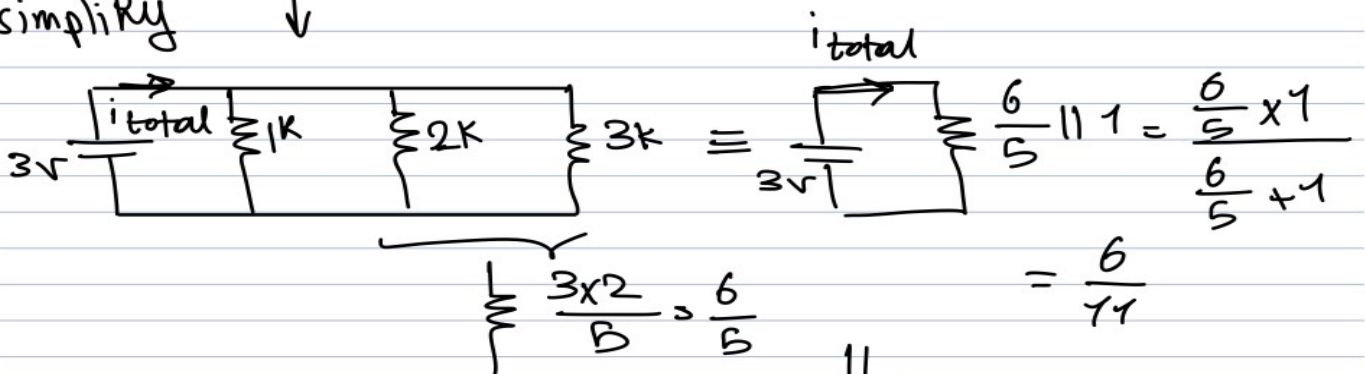

$$i_{total} = \frac{3}{\frac{6}{11}} = \frac{11}{2} = 5.5A$$

$$\Rightarrow I_A = 5.5A \times \frac{\frac{6}{5}}{\frac{6}{5} + 1} = 3mA$$

$$I' = 5.5A \times \frac{1}{1 + \frac{6}{5}} = 2.5mA$$



$$\Rightarrow I_B = I_C = 2.5 \times \frac{3}{5} = 1.5mA$$

$$I_D = I_E = I_F = 2.5 \times \frac{2}{5} = 1mA$$

$$V_A = V_B = V_D = 3V$$

$$V_C = 1.5V, V_E = 2V, V_F = 1V$$

Q4:

a) no current flows since $V_{\text{source}} < V_{\text{th}}$

$$I_D = 0$$

b) From the LED characteristic:

$$I_{\text{diode}} = I_R = 5 \text{ mA} \longrightarrow V_F = 2 \text{ V}$$

$$V_{\text{source}} = V_F + V_{\text{Resistor}} = 2 + RI = 2 + 100 \times 5 \times 10^{-3} \Rightarrow$$

$$V_{\text{source}} = 2.5 \text{ V}$$

Optical power emitted = Power emitted per electron \times number of electrons
 Energy of a single photon = $\frac{hc}{\lambda} = \frac{6.62 \times 10^{-34} \times 3 \times 10^8}{630 \times 10^{-9}} = 3.15 \times 10^{-19} \text{ J}$


$$E_{\text{photon}} = E_{\text{electron}} \Rightarrow I = qn \Rightarrow \frac{5 \times 10^{-3}}{1.6 \times 10^{-19}} = 3.125 \times 10^{16} \frac{\text{electron}}{\text{s}}$$

$$n_{\text{photon}} = \eta \times n_{\text{electron}} = \frac{2}{10} \times 3.125 \times 10^{16} = 6.242 \times 10^{15}$$

$$P_{\text{optical}} = E \times n_{\text{photon}} = 3.15 \times 10^{-19} \times 6.24 \times 10^{15} = 1.96 \times 10^{-3} = 1.9 \text{ mW}$$

Q5:

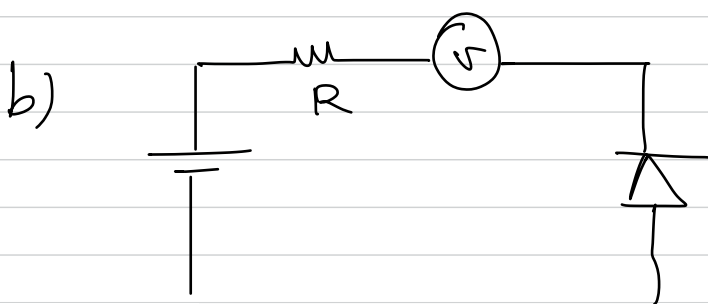
a) the left configuration is more effective in capturing light since it is in reversed bias. In reversed bias the depletion region is widened, which allows it to capture light effectively.



$$V = RI \Rightarrow I_{\text{ph}} = \frac{V_R}{R}$$

we measure Volt through Volt meter & we know the value of R

Q6:

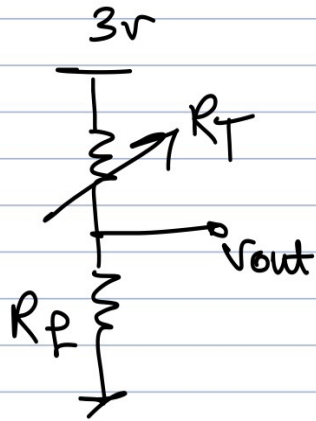

$$R_T = f(v_{out}) \Rightarrow$$


$$v_{out} = R_F \cdot I$$

$$3 = (R_T + R_F) I \Rightarrow$$

$$R_T = \frac{3}{I} - R_F \Rightarrow R_T = \frac{3R_F}{v_{out}} - R_F \Rightarrow$$

$$R_T = R_F \left(\frac{3}{v_{out}} - 1 \right)$$

Q7:

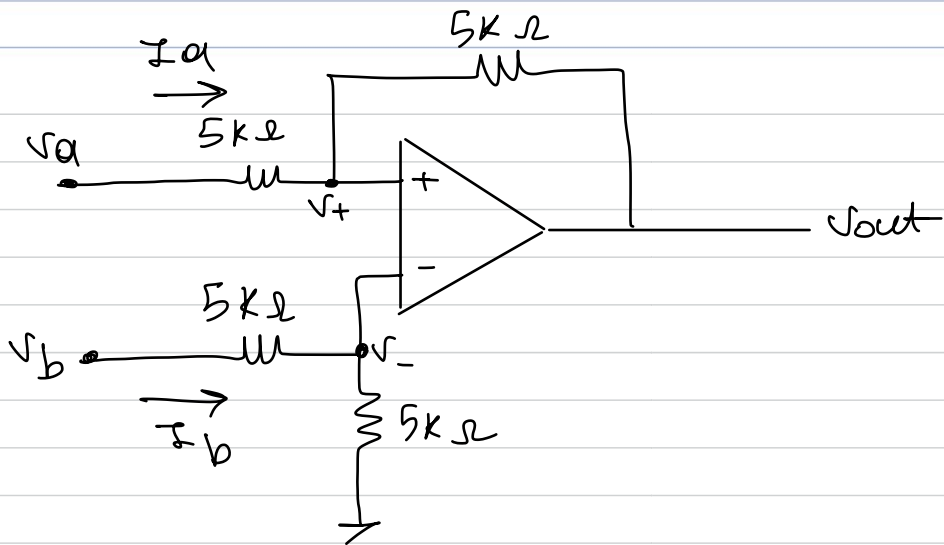

a)

$$v_+ = v_- \Rightarrow v_- = 5I_b = \frac{v_b}{2}$$

$$I_b = \frac{v_b - v_-}{5}$$

$$v_b = 10I_b \Rightarrow I_b = \frac{v_b}{10}$$

$$b) \quad v_a - v_+ = 5I_a \Rightarrow I_a = \frac{v_a - v_+}{5}$$

$$v_+ - v_{out} = 5I_f \Rightarrow I_f = \frac{v_+ - v_{out}}{5}$$

we know $v_+ = v_- \Rightarrow I_a = \frac{v_a - \frac{v_b}{2}}{5} = \frac{2v_a - v_b}{10^k}$

$$I_f = \frac{\frac{v_b}{2} - v_{out}}{5} = \frac{v_b - 2v_{out}}{10^k}$$

$$c) \quad \left. \begin{array}{l} v_{out} = \frac{v_b}{2} - 5I_f \\ I_a = I_f \Rightarrow \frac{v_a - \frac{v_b}{2}}{5} \end{array} \right\} \Rightarrow v_{out} = \frac{v_b}{2} - 5 \left(\frac{v_a - \frac{v_b}{2}}{5} \right) \Rightarrow$$

$$v_{out} = \frac{v_b}{2} - v_a + \frac{v_b}{2} = v_b - v_a$$

$$d) \quad v_{out} = v_b - v_a$$

↓

the circuit perform a difference operation between the input voltages, It's a form of differential amplifier with $R_f = R_a$

$$Q8: I = I_0 \left(e^{\frac{qV}{nKT}} - 1 \right) \Rightarrow$$


$$I_{\min} = 0 \Rightarrow e^{\frac{qV}{nKT}} = 1 \Rightarrow \frac{qV}{nKT} = \ln(1) = 0 \Rightarrow V = 0_{\min}$$

$$I_{\max} = 10 \times 10^{-3} = 1 \times 10^{-2} \times e^{\frac{qV}{nKT}} \Rightarrow$$

$$e^{\frac{qV}{nKT}} = 10^{19} \Rightarrow \frac{qV}{nKT} = 19 \ln(10) = 43.74$$

$$\Rightarrow V = 2 \times 1.38 \times 10^{-23} \times 300 \times 43.74 \times \frac{1}{1.6 \times 10^{-19}} \Rightarrow$$
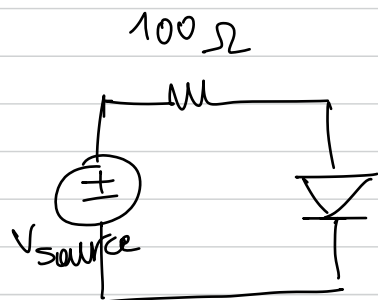
$$V_{LED} = 2.26 \times 10^4 \times 10^{-23} \times 10^{19} = 2.26 \text{ V}$$



$$V_{\text{source}} = V_R + V_{LED} \Rightarrow$$

$$V_R = R \times I = 100 \times 10 \times 10^{-3} = 1 \text{ V}$$

$$V_{\text{source max}} = 1 + 2.26 = 3.26$$

$$V_{\text{source min}} = 0$$

$$b) \text{ Photon Energy: } E = \frac{hc}{\lambda} = \frac{6.62 \times 10^{-34} \times 3 \times 10^8}{532 \times 10^{-9}} = 3.73 \times 10^{-19} \text{ J}$$

$$\text{electrons per second: } I = nq \Rightarrow n = \frac{10 \times 10^{-3}}{1.6 \times 10^{-19}} = 6.25 \times 10^{16} \text{ e}^{-} \text{ s}^{-1}$$


$$\text{photons per second: } n_{\text{photon}} = \eta \times n_{\text{electron}} = 0.43 \times 6.25 \times 10^{16} \\ = 2.68 \times 10^{16} \frac{\text{photons}}{\text{s}}$$

Optical power $\Rightarrow P = n_{\text{photon}} \times E = 2.68 \times 10^{16} \times 3.73 \times 10^{-19} = 10.04 \text{ mW}$

$I_{\text{photodiode}} = R_{\lambda} \times P_{\text{optical}} \rightarrow$ based on the curve $R_{\lambda} \cong 0.3 \frac{\text{A}}{\text{W}}$

$I_{\text{ph}} = 0.3 \times 10.04 \times 10^{-3} = 0.003 = 3 \text{ mA}$

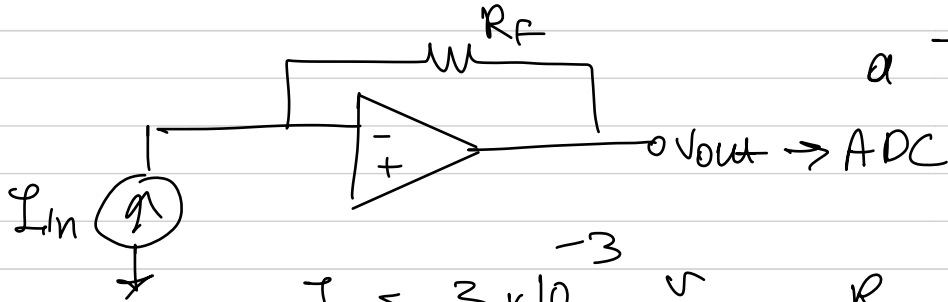Now we need to convert this current to 10 V using a Transimpedance Amplifier.



$$I = 3 \times 10^{-3} = \frac{V}{R} \Rightarrow R = \frac{10}{3 \times 10^{-3}} = 3.3 \text{ k}\Omega$$

We need $R_f = 3.3 \text{ k}\Omega$ but we want to design our circuit using 100Ω resistors so we need 33, 100Ω resistors in series.