
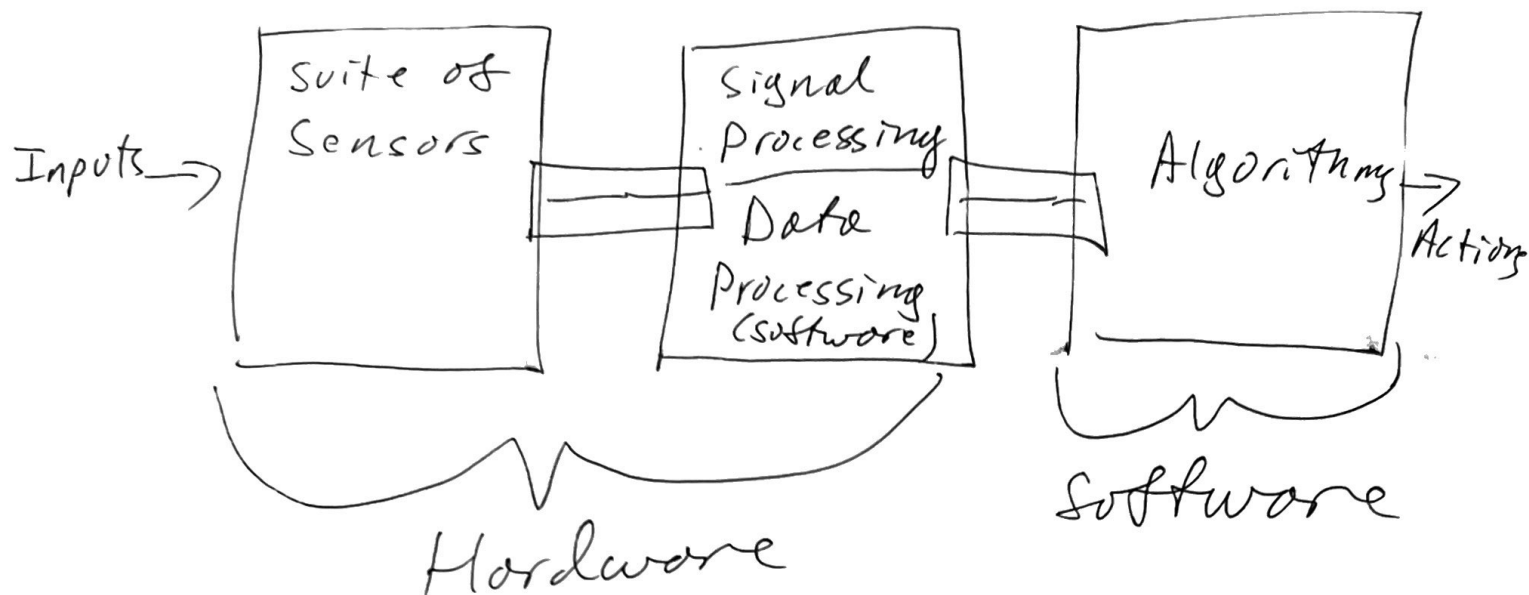


um ~~4/17~~ Systems

⑥

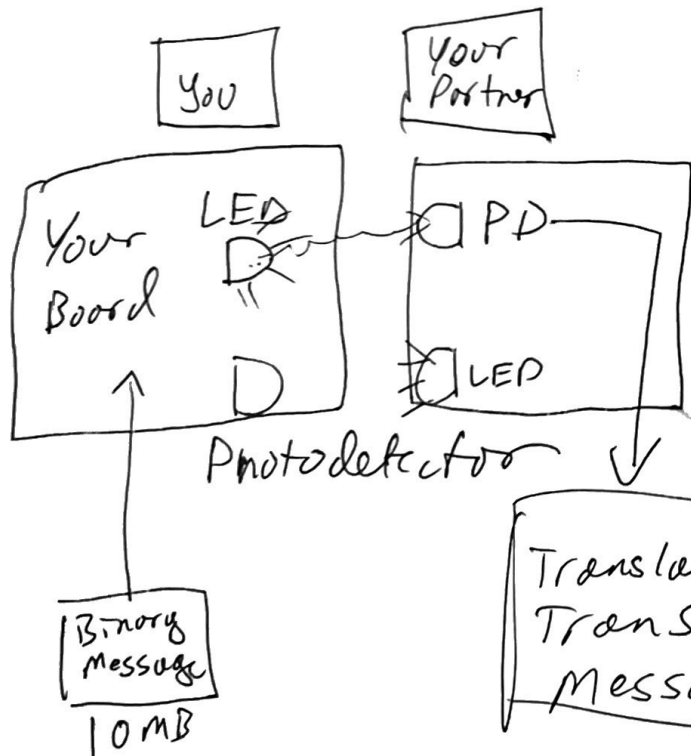

I-E 105 Challenge #1





HW grade

Transmit message
w/ > 95% accuracy


Competition

- Who can transmit in the shortest time period.
- Highest data rate

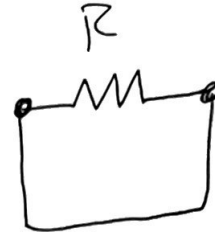
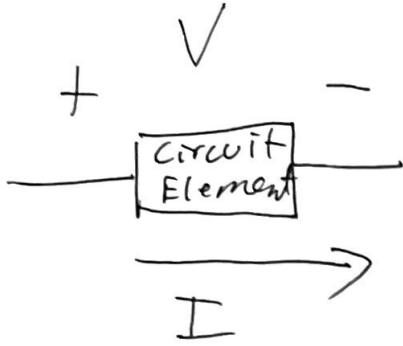
- ① Voltage: Pressure that leads to current flow
 Current: movement of charge
 Resistor: A circuit element that has a linear proportionality between current & voltage



Ohm's Law: $V = IR$

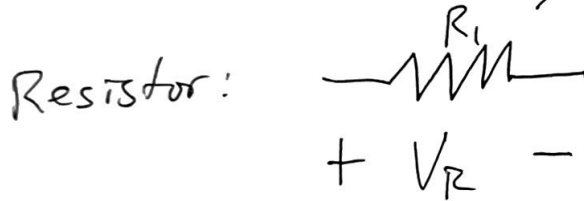





$$\frac{V_R}{R_1} = I$$

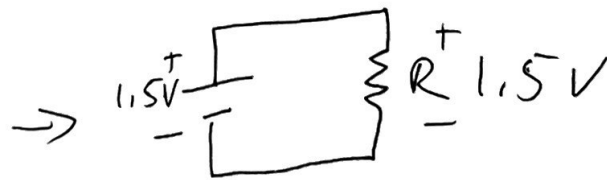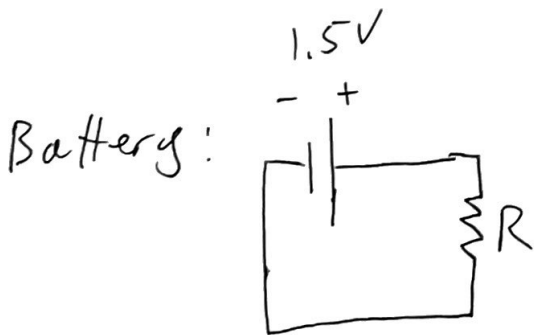

$$R = 1.5 \Omega$$

$$I = 1 A = 1 \frac{C}{s}$$

2

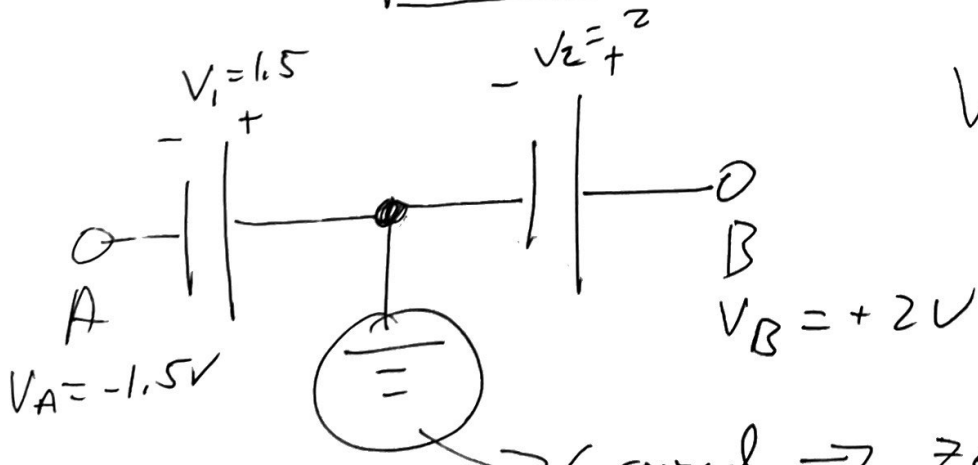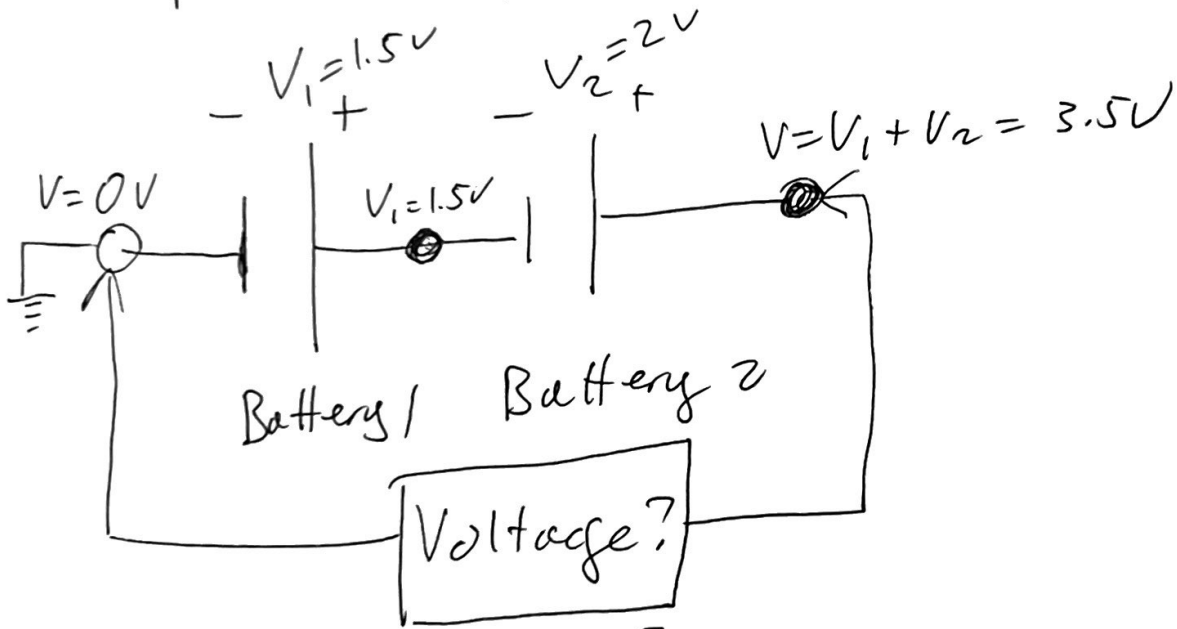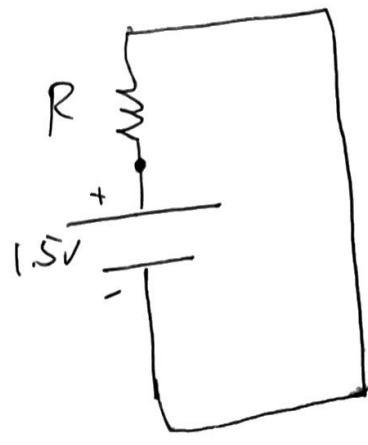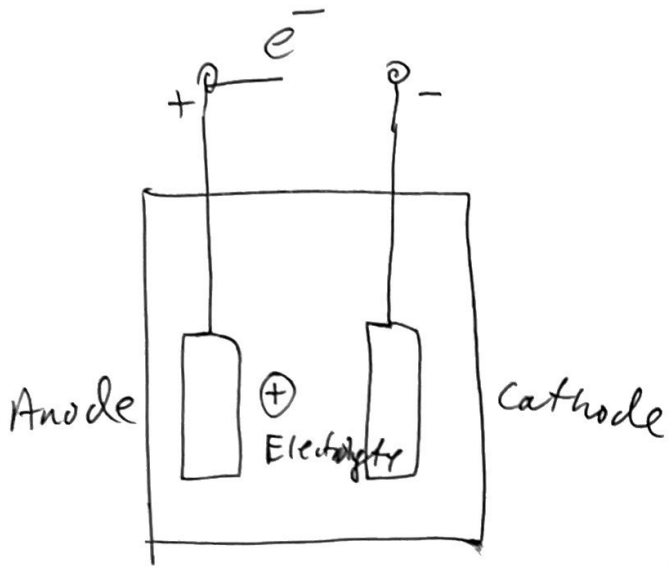

$V_A = 0?$
 $= -1.5V?$


Ground \rightarrow Zero Voltage Reference

Voltage

③

① Voltage source enforces a voltage difference across 2 points.

② Voltage sources in series add

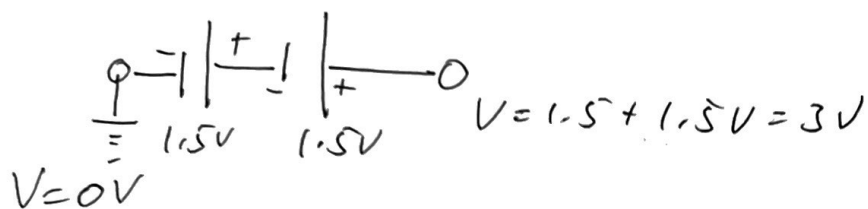

③ A ~~circuit~~ circuit element enforces some specific $I-V$ relationship

④ A resistor has the $I-V$ relationship


$$V = IR \text{ (Ohm's Law)}$$

Current

• The flow of charge


• The unit for current is the Amp, which
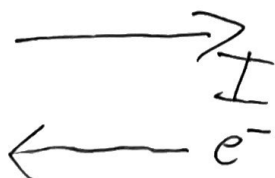
$$I = \frac{\text{Charge}}{\text{time}} = \frac{\text{Coulomb}}{s}$$



④


$R = 1.5 \Omega$

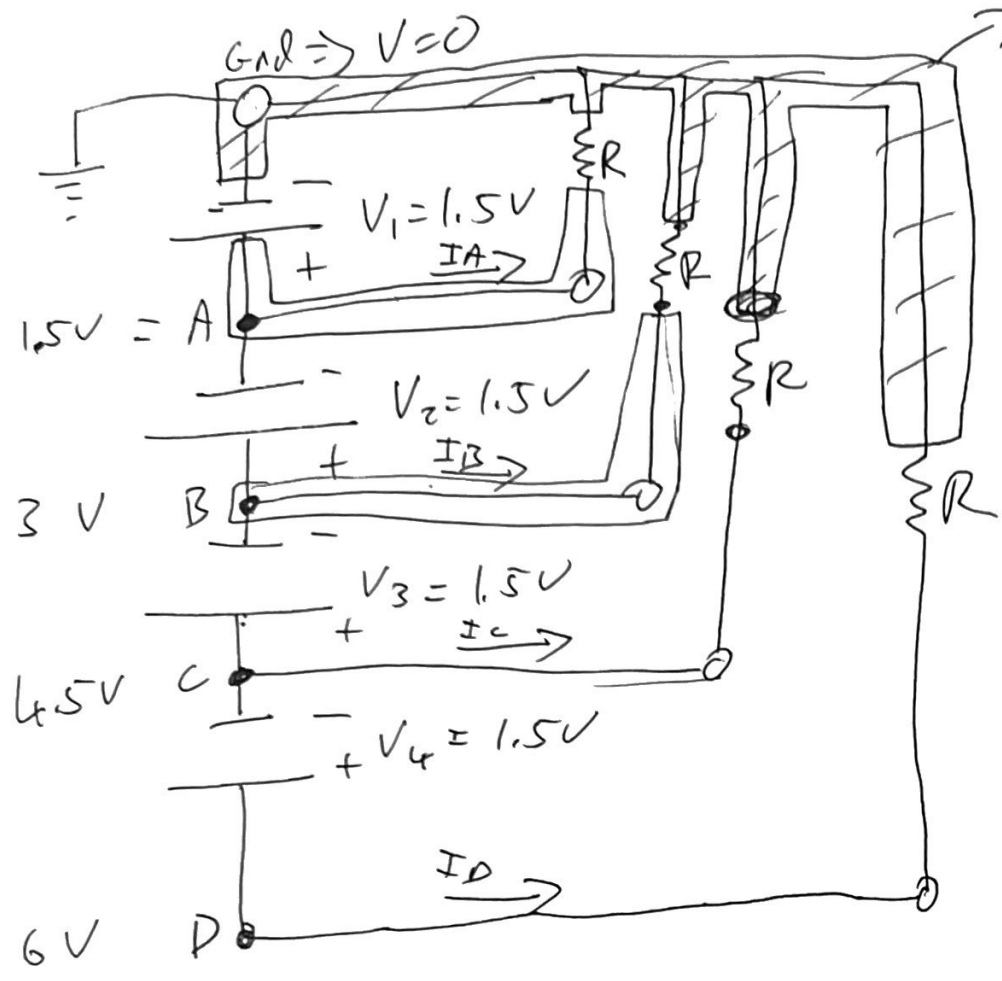

$V = 0V$


$V_A = 1.5V$
 $V_B = 3V$
 $V_C = 4.5V$
 $V_D = 6V$

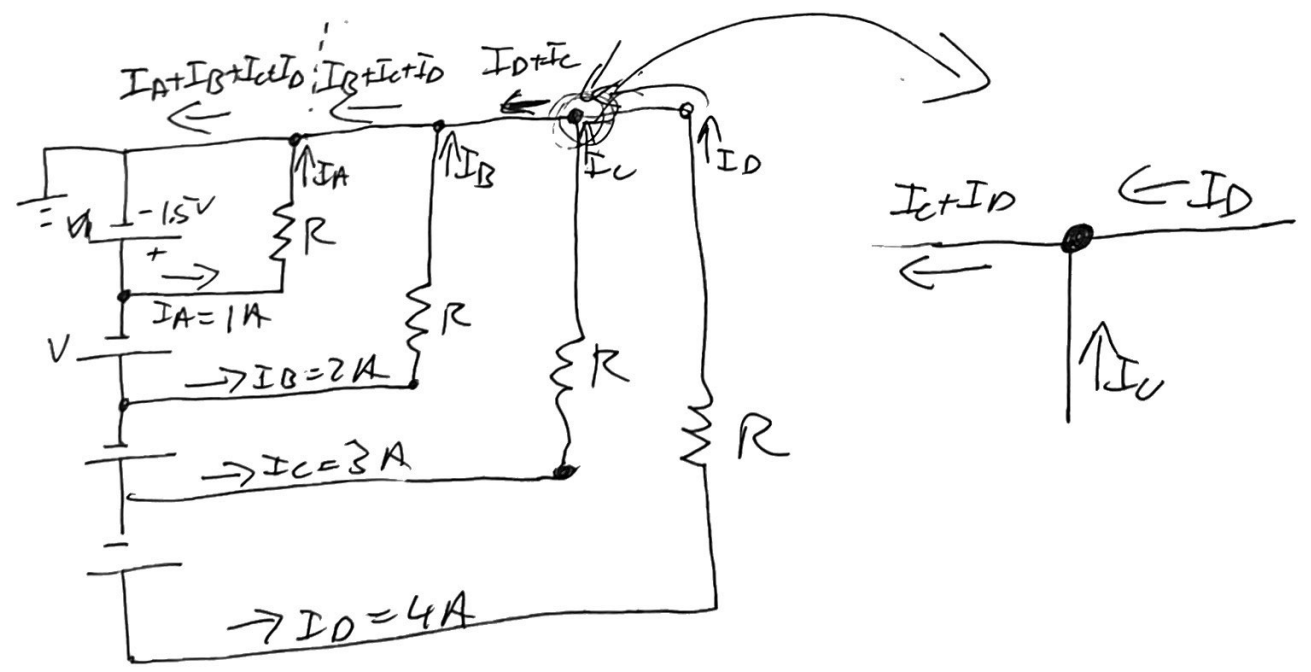$I_A = \frac{1.5V}{1.5\Omega} = 1A$
 $I_B = \frac{3V}{1.5\Omega} = 2A$
 $I_C = \frac{4.5V}{1.5\Omega} = 3A$
 $I_D = \frac{6V}{1.5\Omega} = 4A$



Kirchhoff's Current Law
 The current entering a node is equal to the current leaving a node



5

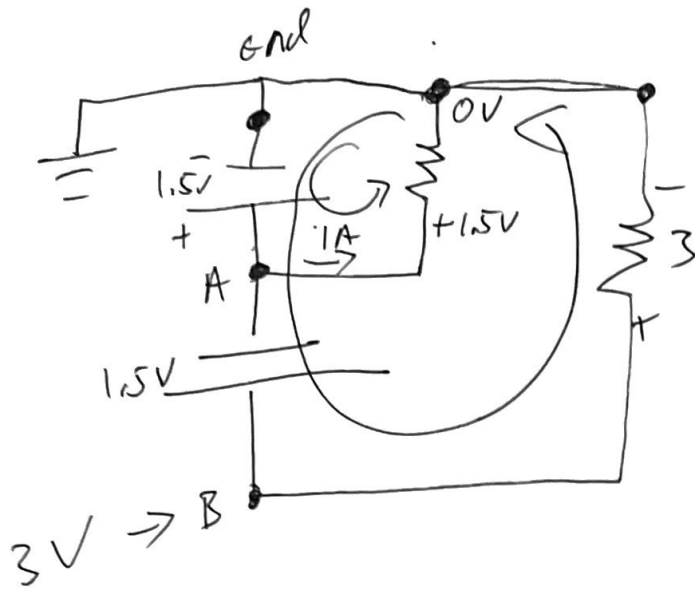

Kirchhoff's Voltage law
The voltage around a
loop in the circuit
is $= 0V$

$$\begin{array}{ccccccc} \text{Gnd} & \rightarrow & A & \rightarrow & B & \rightarrow & \text{Gnd (via resistor)} \\ & & +1.5V & & +1.5V & & -3V \\ & & V=3V & & V_{\text{Tot}} = 1.5 + 1.5 - 3 = 0 \end{array}$$



Resistors

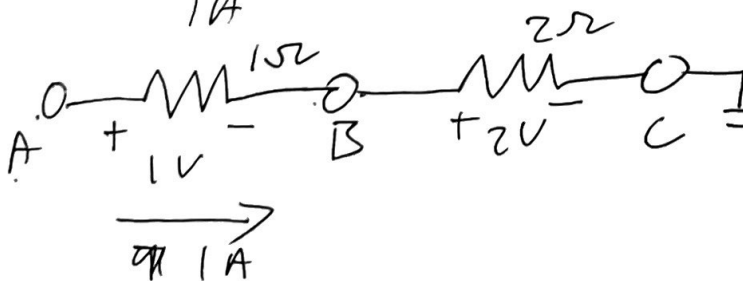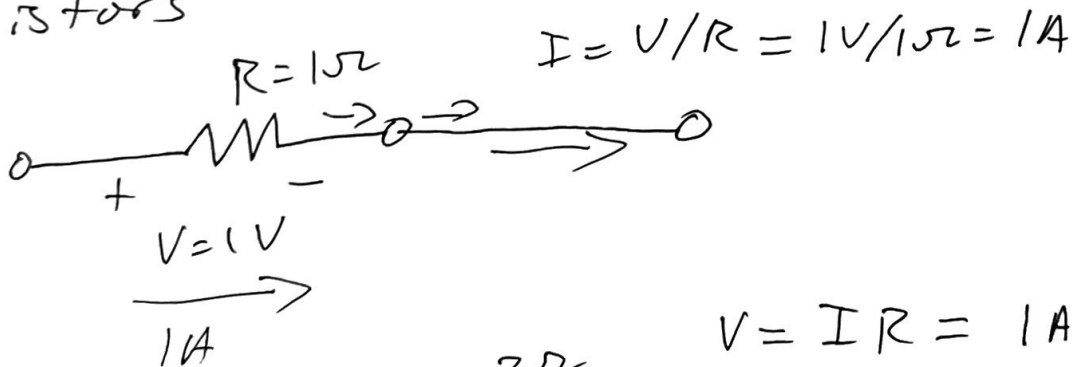


$$V = IR = 1A \cdot 2\Omega = 2V$$

$$V_A - V_C = ?$$


$$3V - 0V = 3V$$

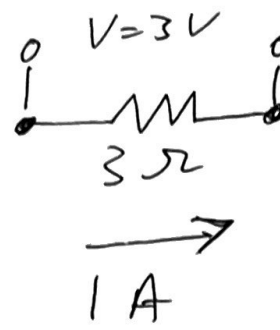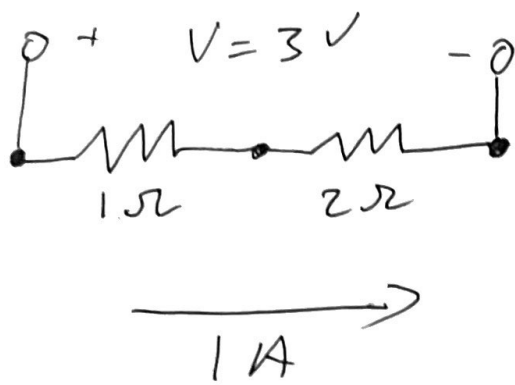

Series Resistors

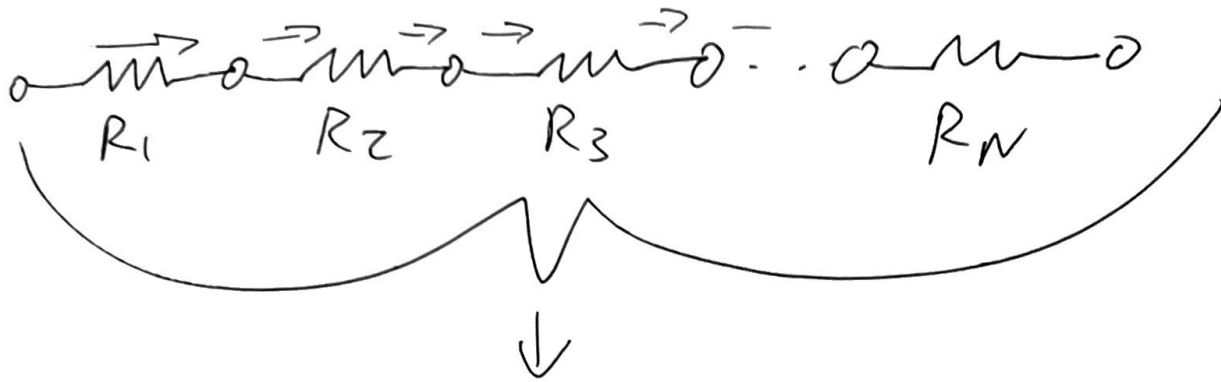
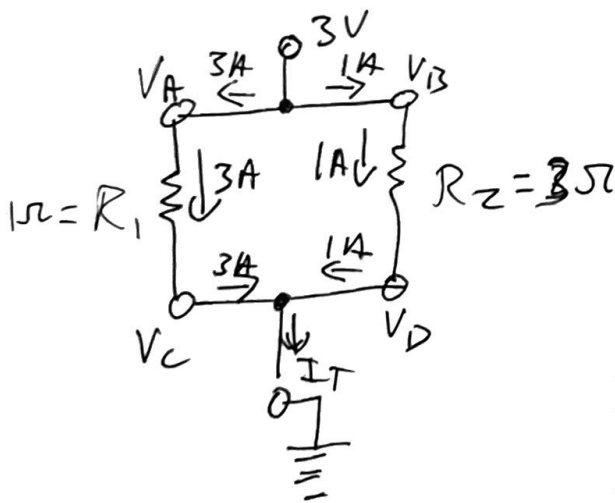
$$R_S = R_1 + R_2 + R_3 + \dots + R_N = \sum_{i=1}^N R_i$$



$$V_A = V_B$$

$$V_C = V_D$$



$$I_{R_1} = 3V / 1\Omega = 3A$$

$$I_{R_2} = 3V / 3\Omega = 1A$$

$$I_{R_1} + I_{R_2} = I_T$$

$$3A + 1A = 4A$$

⑦

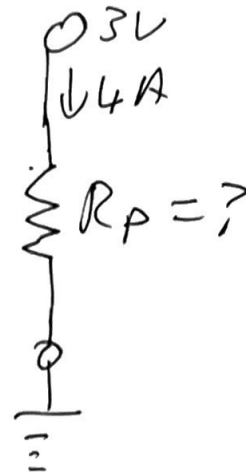
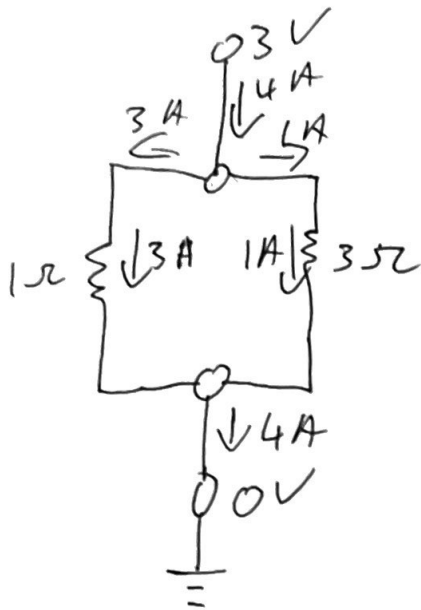


$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{3V}{4A}$$

$$0.75\Omega =$$

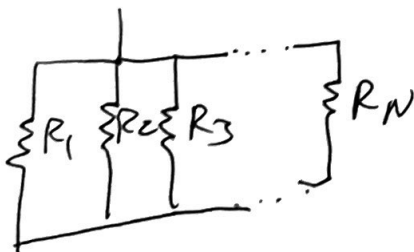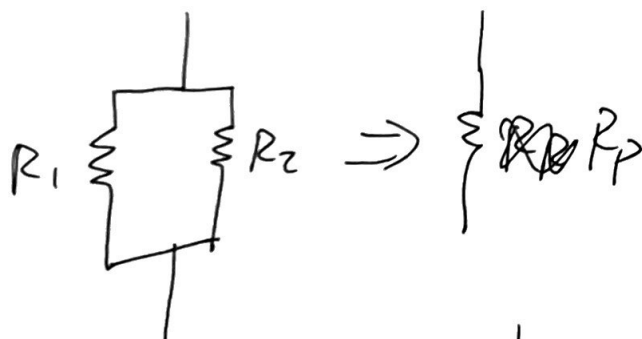

$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_P} = \frac{1}{1\Omega} + \frac{1}{3\Omega} = \frac{4}{3} \frac{1}{\Omega}$$

$$\frac{1}{R_P} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N} \right) \quad R_P = \frac{3}{4} \Omega$$

$$\frac{1}{R_P} = \sum_{i=1}^N \frac{1}{R_i}$$

$$R_P = \left(\sum_{i=1}^N \frac{1}{R_i} \right)^{-1}$$

Voltage \Rightarrow Pressure ; Voltage sources define a voltage diff across 2 pts. (8)

Current \Rightarrow moving Chg

Resistors $\Rightarrow V=IR$

Kirchoff's Current Law:

- The currents going into a node = the currents exiting a node
- All the currents entering a node = 0

$$KCL \quad \sum_{i=1}^N I_i = 0$$

Kirchoff's Voltage Law:

- The voltages around a loop in the circuit = 0 V

$i=1, 2, 3, 4, \dots$

$$\sum_{i=1}^N V_i = 0$$

- Series Resistors : $R_s = \sum_{i=1}^N R_i = R_1 + R_2 + R_3 + \dots$
- Parallel Resistors : $R_p = \left(\sum_{i=1}^N \frac{1}{R_i} \right)^{-1}$

