

ECE 105: Introduction to Electrical Engineering


Lecture 13

Sensors 1

Yasser Khan


Rehan Kapadia

What is a sensor?

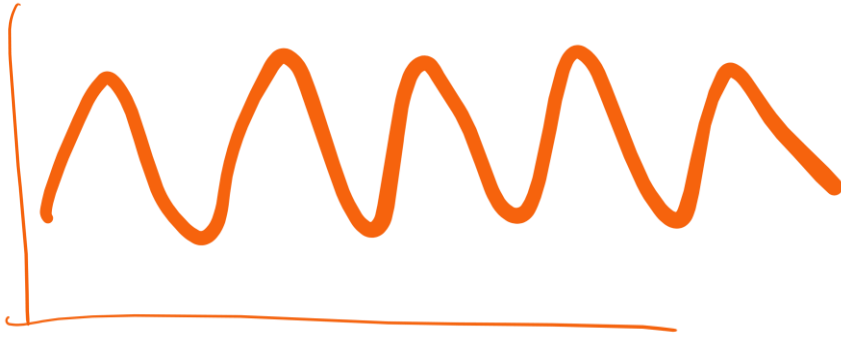




What is a sensor?

physical → electrical signal

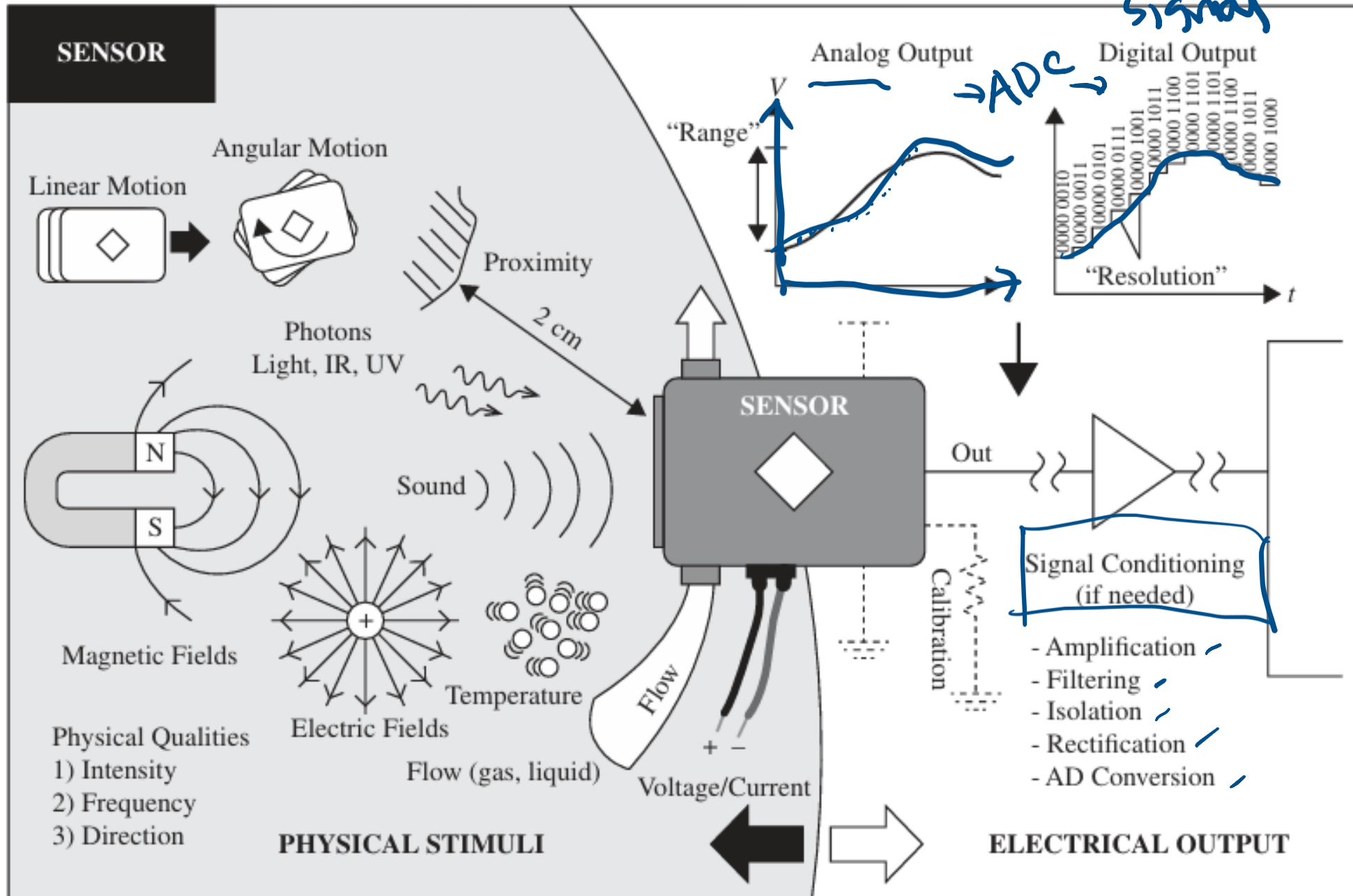


Sensors in circuits:




How sensors are used in circuits:

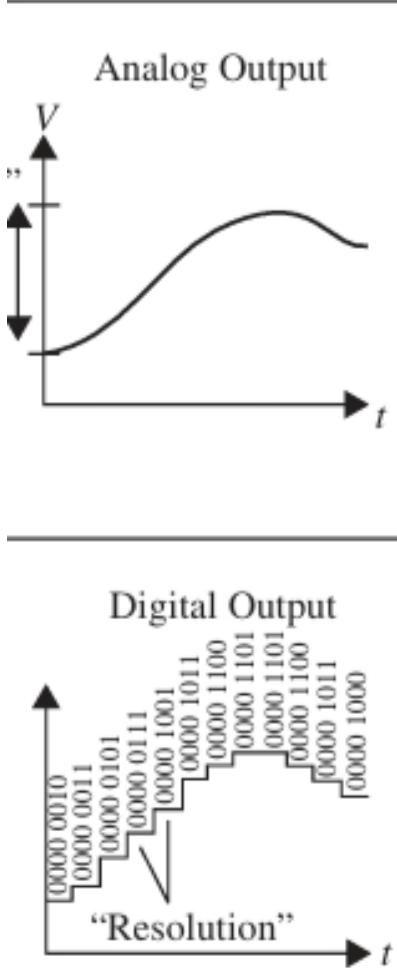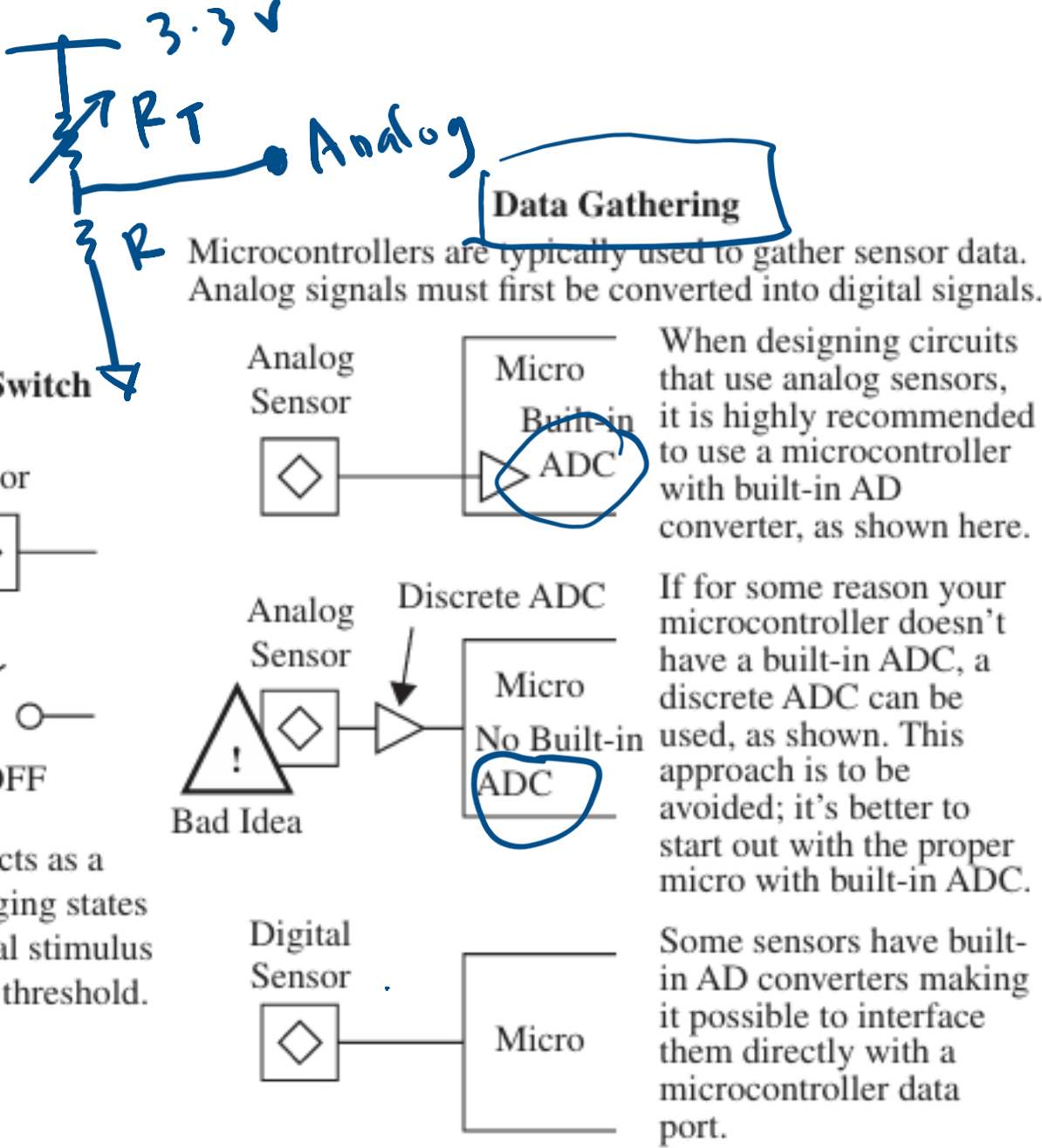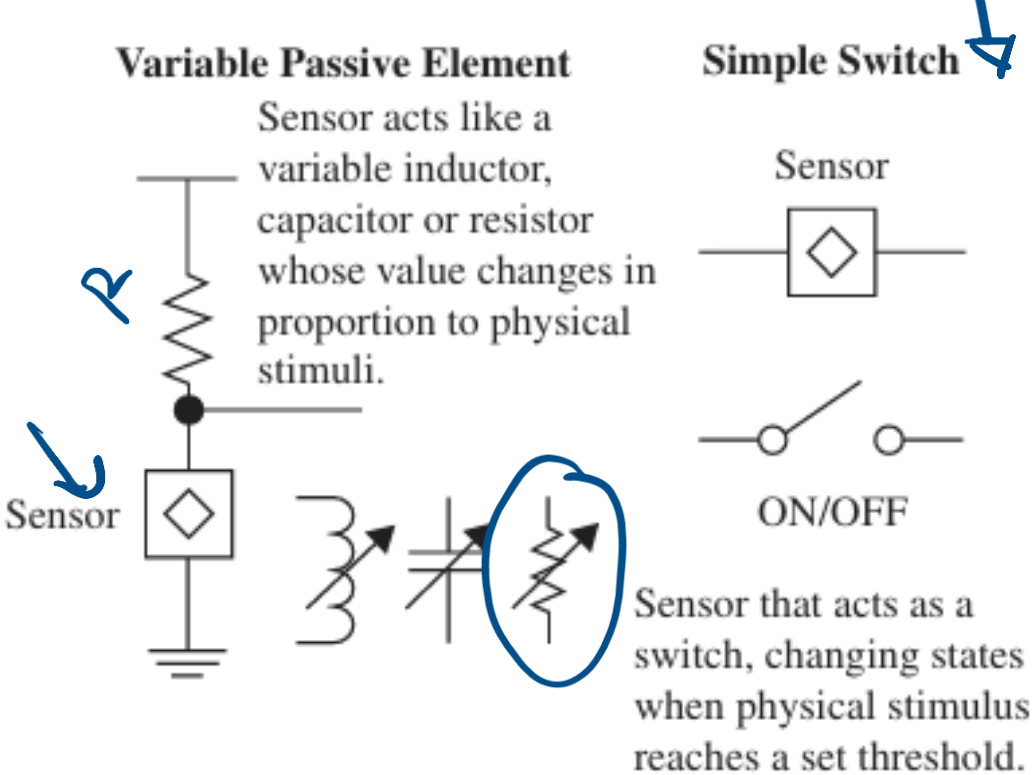

Types of sensors

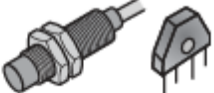TYPES OF SENSORS			Sensors in bold are covered in this chapter.	
Category of Sensor		What It Does	Example Devices	
Position Measuring Devices		Designed to detect and respond to changes in angular position or in linear position of the device.	Potentiometer Linear Position Sensor Hall Effect Position Sensor Magnetoresistive Angular	Encoders: -Quadrature -Incremental Rotary -Absolute Rotary -Optical
Proximity, Motion Sensors		Designed to detect and respond to movement outside of the component but within the range of the sensor.	Ultrasonic Proximity Optical Reflective Optical Slotted PIR (Passive Infrared)	Inductive Proximity Capacitive Proximity Reed Switch Tactile Switch
Inertial Devices		Inertia Devices designed to changes in the physical movement of the sensor.	Accelerometer Potentiometer Inclinometer Gyroscope Vibration Sensor/Switch	Tilt Sensor Piezo Shock Sensor LVDT/RVDT
Pressure/Force		Pressure Devices designed to detect a force being exerted against it.	IC Barometer Strain Gauge Pressure potentiometer LVDT Silicon transducer	Piezoresistive sensor Capacitive transducer
Optical Devices		Optical Devices designed to detect the presence of light or a change in the amount of light on the sensor.	LDR Photodiodes Phototransistors Photo interrupters Reflective Sensors	IrDA Transceiver Solar Cells LTV (Light to Voltage) Sensors

Types of sensors

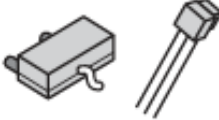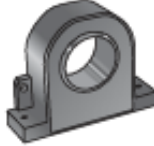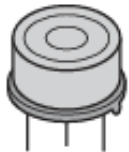Image, Camera Devices		Image, Camera Devices designed to detect and change a viewable image into a digital signal.	CMOS Image Sensor
Magnetic Devices		Magnetic Devices designed to detect and respond to the presence of a magnetic field.	Hall Effect sensor Magnetic Switch Linear Compass IC Reed Sensor
Media Devices		Media Devices designed to detect and respond to the presence or the amount of a physical substance on the sensor.	Gas Smoke Humidity, Moisture Dust Float Level Fluid Flow
Current and Voltage Devices		Current Devices designed to detect and respond to changes in the flow of electricity in a wire or circuit.	Hall Effect current sensor DC current sensor AC current sensor Voltage Transducer
Temperature		Temperature Devices designed to detect the amount of heat using different techniques and in different mediums.	Thermistor NTC Thermistor PTC Resistance Temp Detectors (RTD) Thermocouple Thermopile Infrared Thermometer/Pyrometer Digital IC Analog IC
Specialized		Specialized Devices designed to provide detection, measurement, or response in specialized situations, which also may include multiple functions.	Audio Microphone Geiger-Müller Tube Chemical

Temperature sensor



Thermistor




TMP36

Transistor




Thermocouple






Sensor calibration

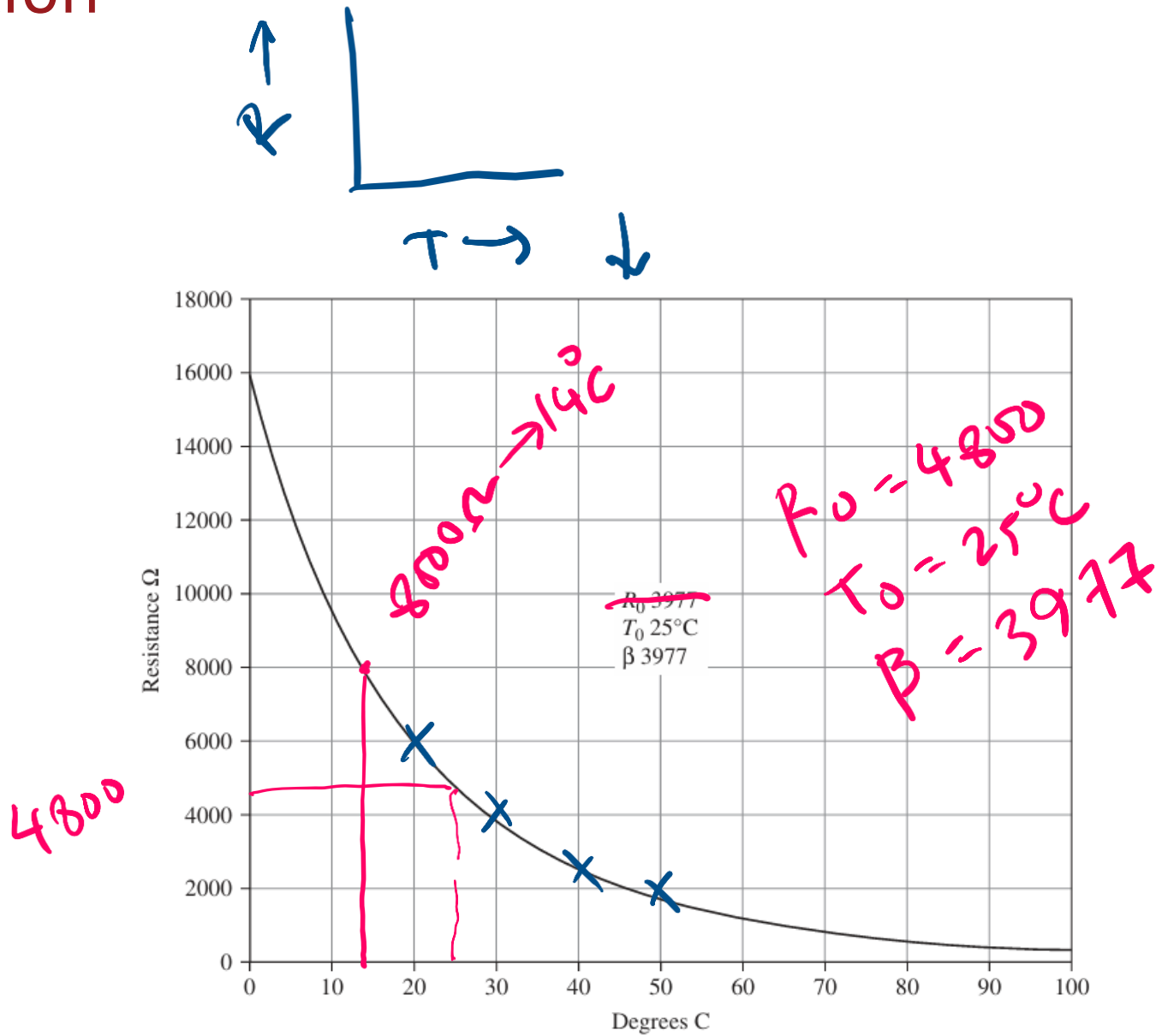

Sensor calibration

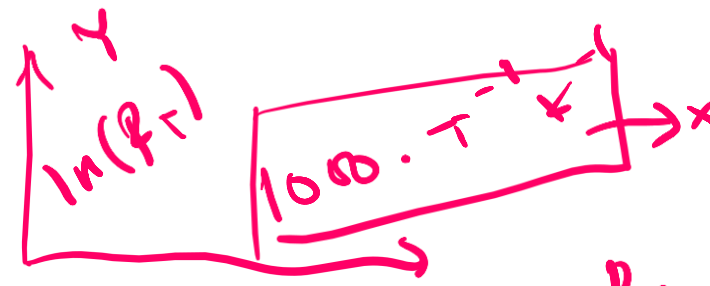
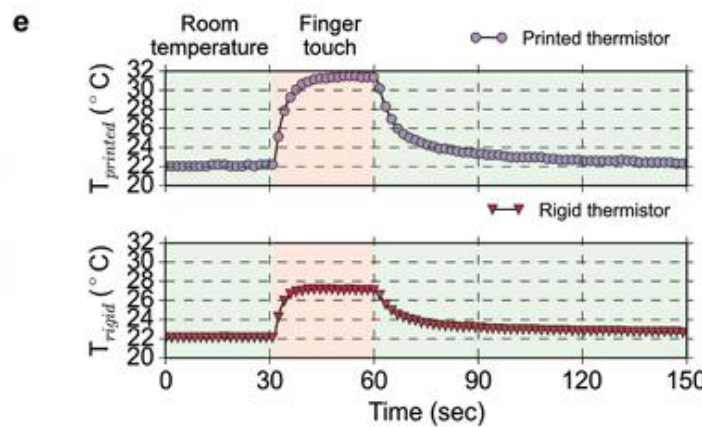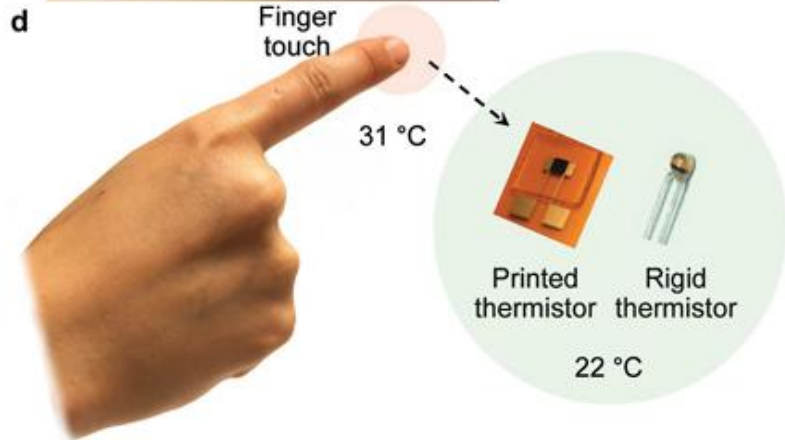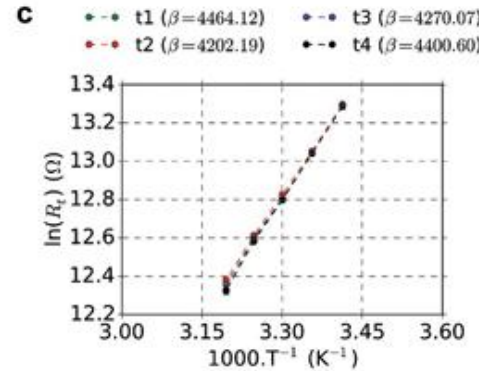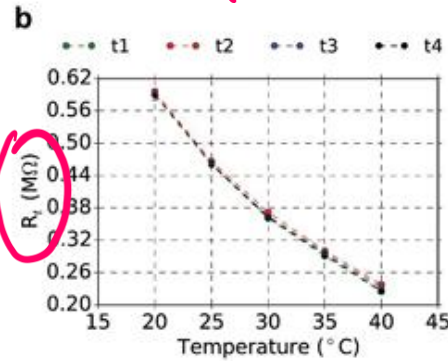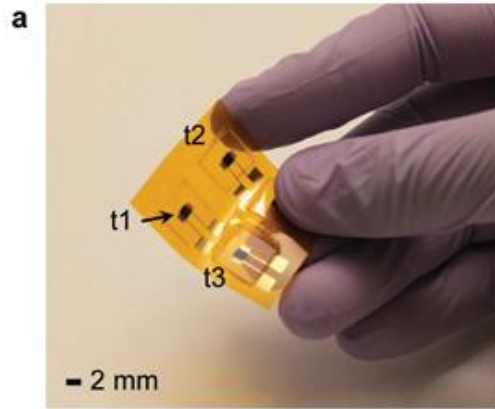
$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{T_0} \right)}$$



$R_T \rightarrow$ comes from ckt


$R_0 \rightarrow$ datasheet

$\beta \rightarrow$ datasheet


$T \rightarrow ?$

$T_0 \rightarrow$ datasheet.


Using sensors in circuits

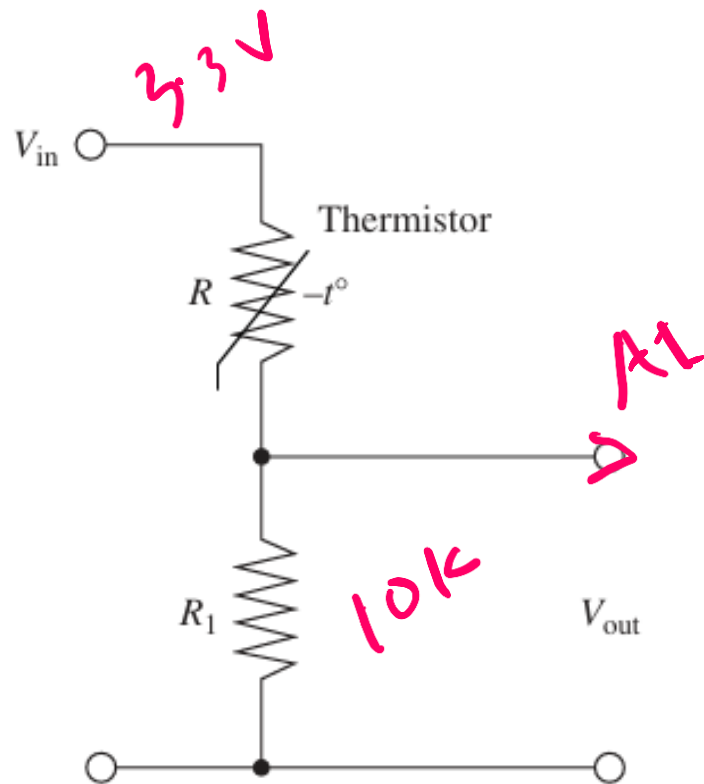

Symbols for Thermistors

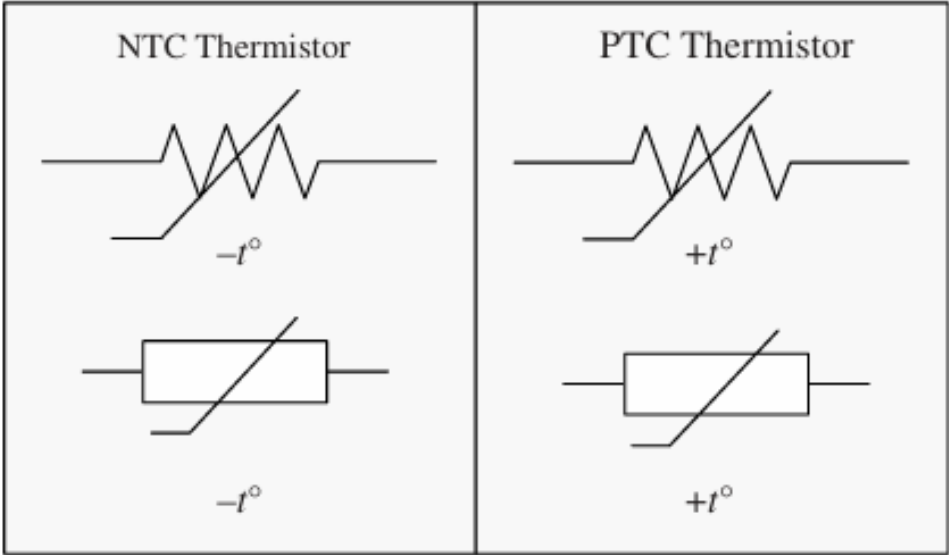

Wheatstone bridge

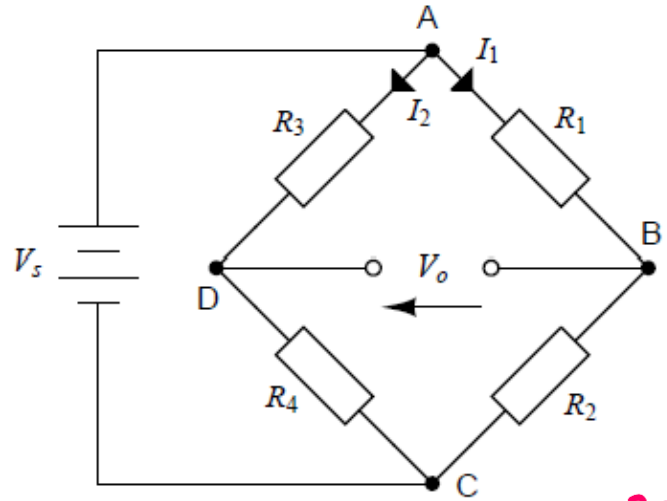

Then $V_o = (V_s - V_{AD}) - (V_s - V_{AB}) = V_{AB} - V_{AD}$ which works o

$$V_o = V_s \left(\frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$

$$V_o = V_s \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)}$$

If V_o is zero we can work back from this to the resistor ratios shown before. However, what if one resistor is a sensor with a resistance that has changed by some value δR ? The new value for the resistor is then $R_x = R_1 + \delta R$ and if this is substituted into Equation the result is:

$$V_o = V_s \frac{(R_1 + \delta R)R_4 - R_2 R_3}{(R_1 + \delta R + R_2)(R_3 + R_4)}$$

Now if we begin with a balanced bridge where all the resistors, including the sensor, have the same value, that is $R_1 = R_2 = R_3 = R_4 = R$ then can be simplified to:


$$V_o = V_s \frac{\delta R}{4R + 2\delta R} \approx V_s \frac{\delta R}{4R}$$

$$V_{AB} = \frac{V_s R_1}{R_1 + R_2}$$

$$V_{AD} = \frac{V_s R_3}{R_3 + R_4}$$



Precise thermistor measurement steps

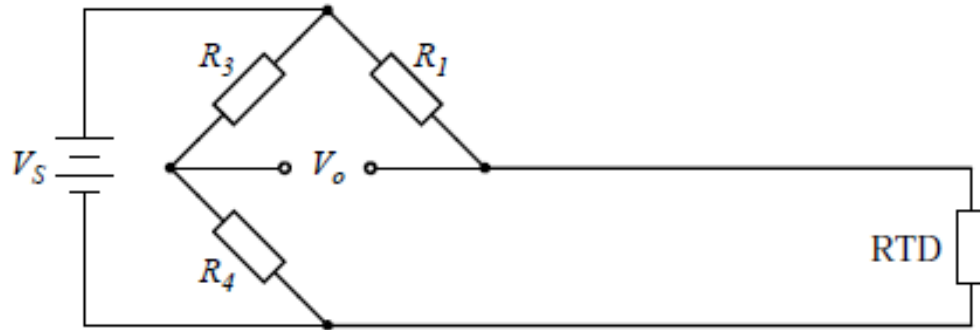

$$R_T = R_0(\alpha A, B, C)$$

$$R_T = R_0[1 + AT + BT^2 + (T - 100)CT^3]$$

for temperatures $-200^\circ\text{C} < T < 0^\circ\text{C}$ and:

$$R_T = R_0[1 + AT + BT^2]$$

for $0^\circ\text{C} < T < 661^\circ\text{C}$.

These equations contain higher order coefficients and these can be found by calibrating the individual resistor. The accepted values for a 'pt100' RTD with a standard temperature coefficient are:


$$A = 3.908310^{-3}\text{K}^{-1}$$

$$B = -5.77510^{-7}\text{K}^{-2}$$

$$C = -4.18310^{-12}\text{K}^{-4}.$$

Sensitivity


$$S_{\text{out}} = f(S_{\text{in}})$$

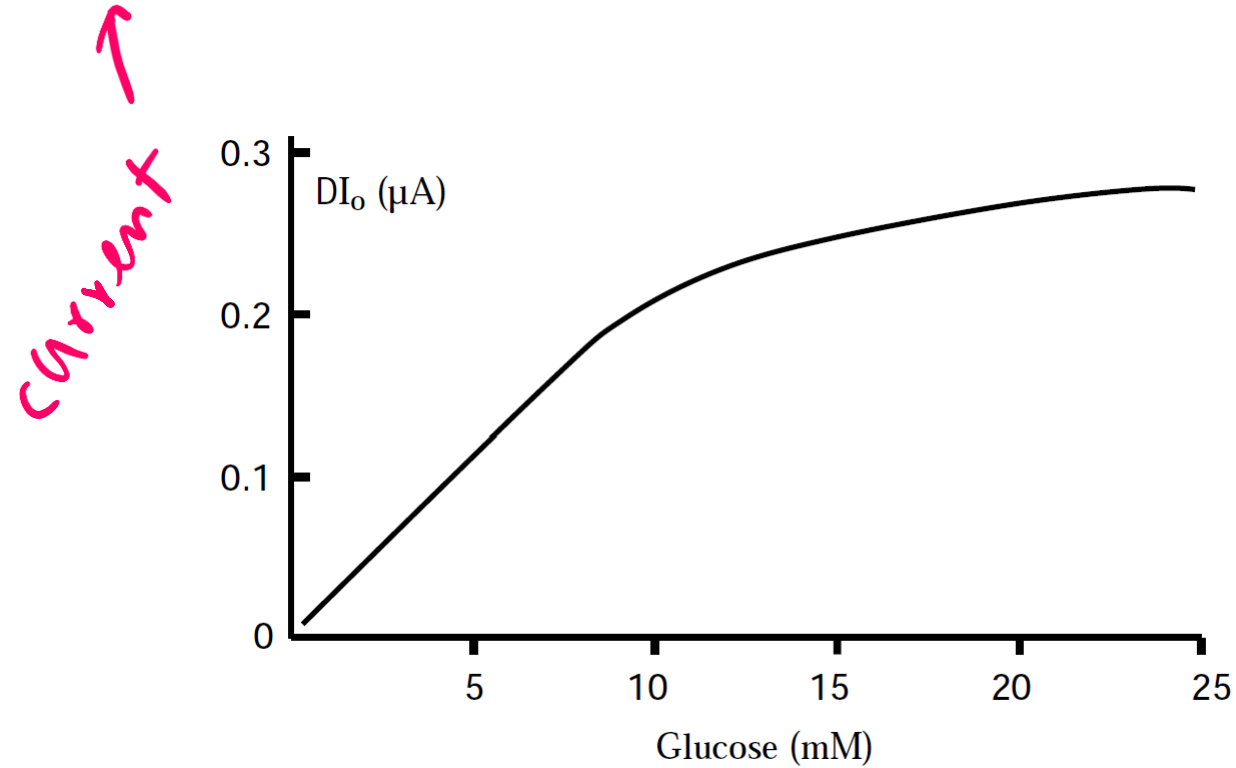

$$\frac{\delta S_{\text{out}}}{\delta S_{\text{in}}}$$

$S = \frac{\Delta \text{current}}{\Delta \text{light}}$

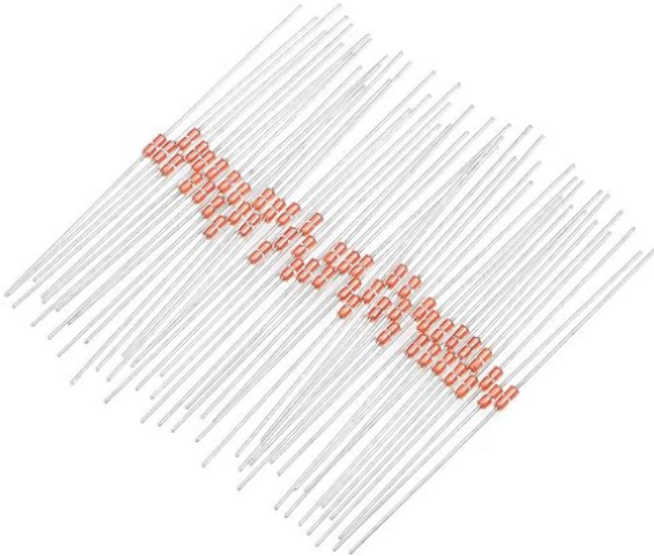Let's build our temperature sensor circuit



Roll over image to zoom in



uxcell 50PCS NTC Thermistors Resistors MF58 3950B 10K Ohm Glass Sealed Temperature Sensors

Visit the uxcell Store

4.7 28 ratings | [Search this page](#)

\$7⁹⁹

Two-Day

FREE Returns

With **Amazon Business**, you would have **saved \$139.37** in the last year. [Create a free account](#) and **save up to 3%** today.

Brand	uxcell
Item dimensions L x W x H	3.54 x 2.36 x 0.39 inches
Measurement Type	Ohmmeter
Manufacturer	uxcell

About this item

- **FEATURES:** MF58 10K Ohm NTC Thermistors with B Value: 3950(+/-1%)
- **DESIGN:** Glass sealed packaging with firm structure, small size and light weight, applicable in severe environments
- **PERFORMANCE:** High precision resistance, B values with high reliability and stability, high sensitivity
- **APPLICATION:** Suitable for related equipment with temperature measurement and controls thermal protection circuits in various family appliances
- **PACKAGE:** 50(+/-2%) Piece x Electrical Axial Lead NTC Thermistors Resistors

Delivery

Pickup

\$7⁹⁹

Two-Day

FREE Returns

FREE delivery **Friday, September 20.** Order within 5 hrs 41 mins

Deliver to Sifat - Rancho Palos... 90275

Only 9 left in stock - order soon.

Quantity: 1


Add to Cart

Buy Now

Ships from Amazon
Sold by uxcell
Returns 30-day refund/replacement
Payment Secure transaction
 See more


What else is needed to create this circuit?

Frequently bought together

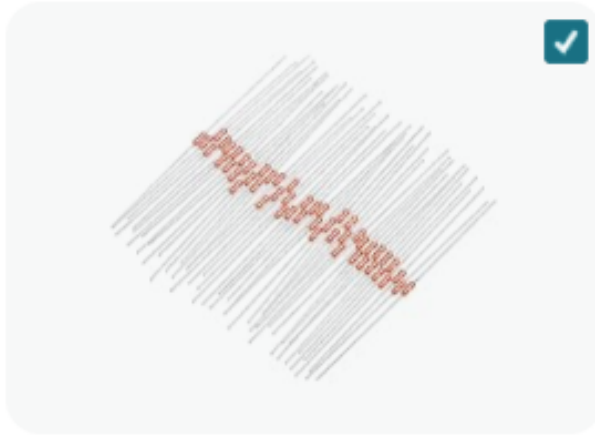



This item: uxcell 50PCS NTC
Thermistors Resistors MF58
3950B 10K Ohm Glass Sealed...

+

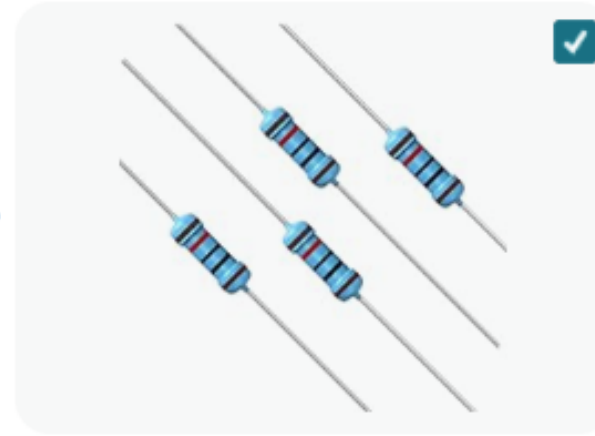

100 PCS 10K ohm Resistor 1/4w
(0.25 Watt) $\pm 1\%$ Tolerance Metal
Film Fixed Resistors, Over 200...

Demo board setup

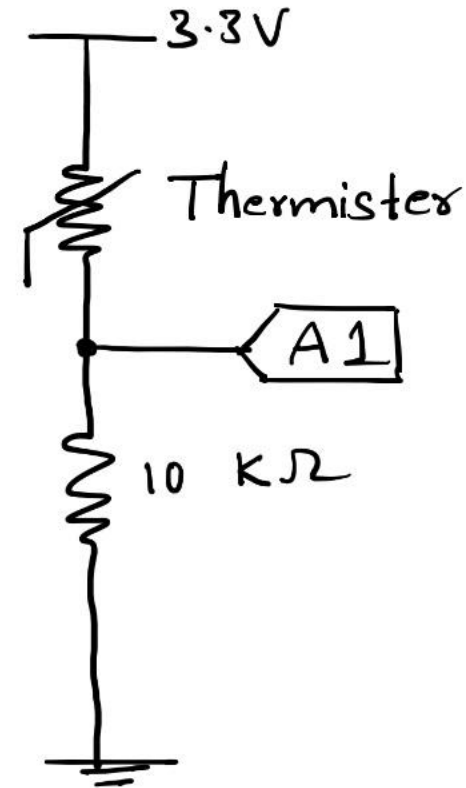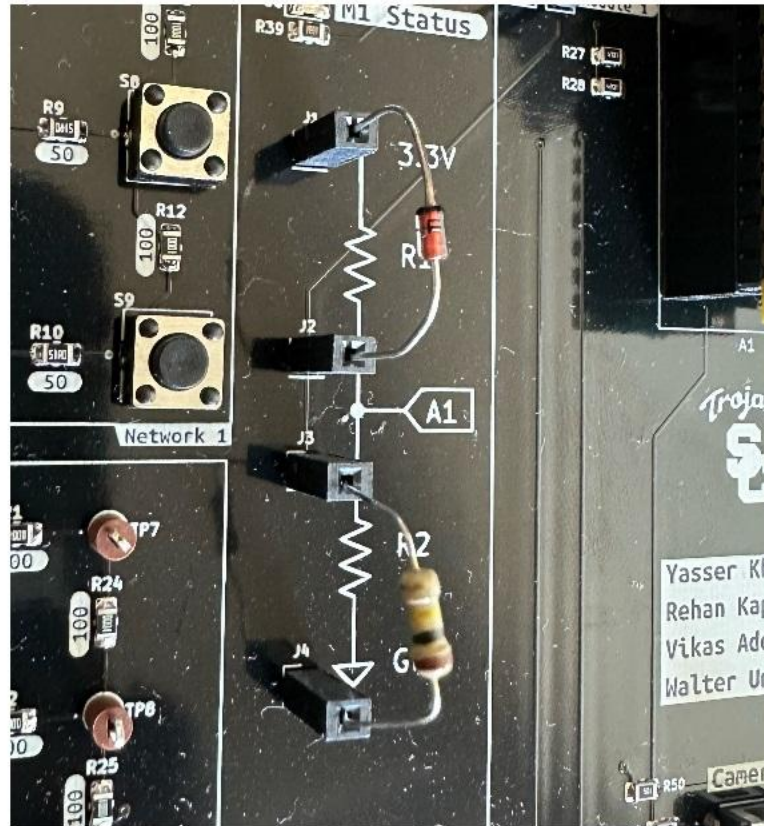

Sensor circuit


Arduino sketch

```
voltage_divider | Arduino IDE 2.3.2
File Edit Sketch Tools Help
Arduino Nano 33 BLE
voltage_divider.ino
1 #include <Arduino.h>
2
3 #define m1_vd_input ? // 1. change here, m1_vd_input ? which ADC is connected to your voltage divider
4 #define adc_resolution 1024
5
6 bool readingEnabled = false;
7 int counter = 0;
8
9 void setup() {
10   Serial.begin(115200);
11   while (!Serial); // Wait for the serial port to be ready (for certain boards like Leonardo)
12 }
13
14 void loop() {
15   // Check if any serial input is available
16   if (Serial.available() > 0) {
17     String command = Serial.readStringUntil('\n'); // Read the command from the serial monitor
18
19     // Check if the entered command is 'readvoltage'
20     if (command == "readvoltage") readingEnabled = true;
21   }
22
23   while(readingEnabled){
24     Serial.println(analogRead(m1_vd_input));
25     counter = counter + 1;
26     if(counter == ?){ // 2. change here, counter == ? for getting 10s
27       counter = 0;
28       readingEnabled = false;
29       Serial.println("Ready to enter next command");
30       break;
31     }
32     delay(1);
33   }
34 }
35
```



Handwritten annotations:

- AI** (pointing to line 3)
- Var** (pointing to line 4)
- Setup** (pointing to the `setup()` function)
- 10000** (pointing to line 26)
- All the time** (pointing to the `while(readingEnabled)` loop)
- (1) what ADC** (pointing to line 3)
- (2) counter = 10s** (pointing to line 26)

Serial plotter

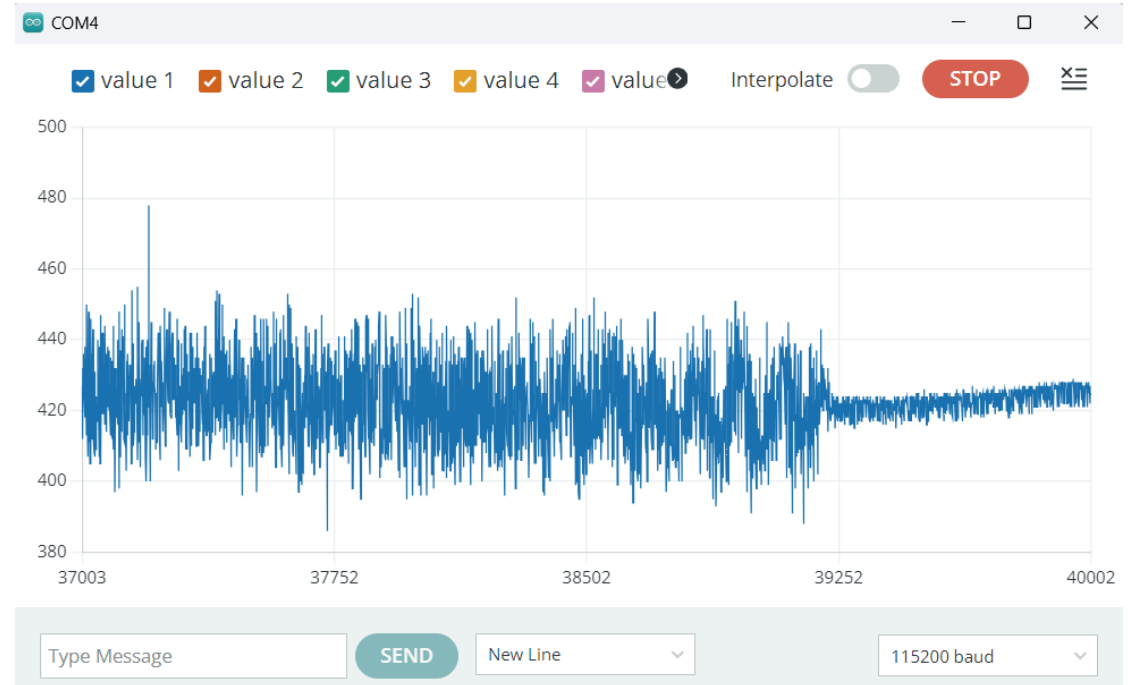

Temperature plots

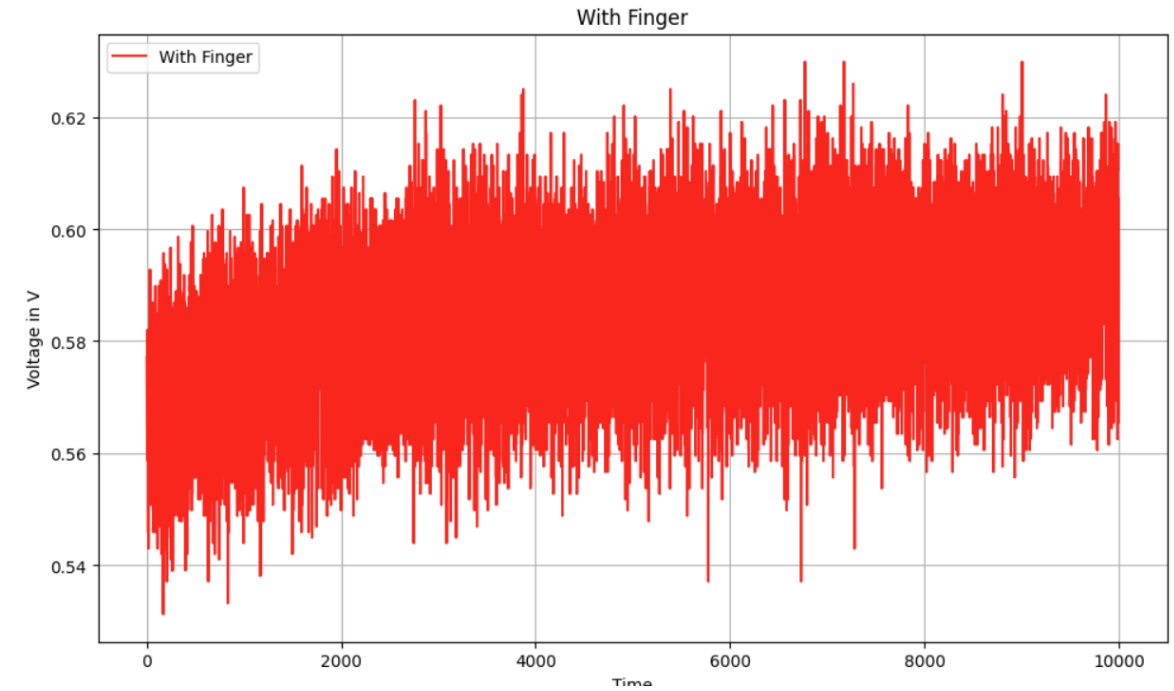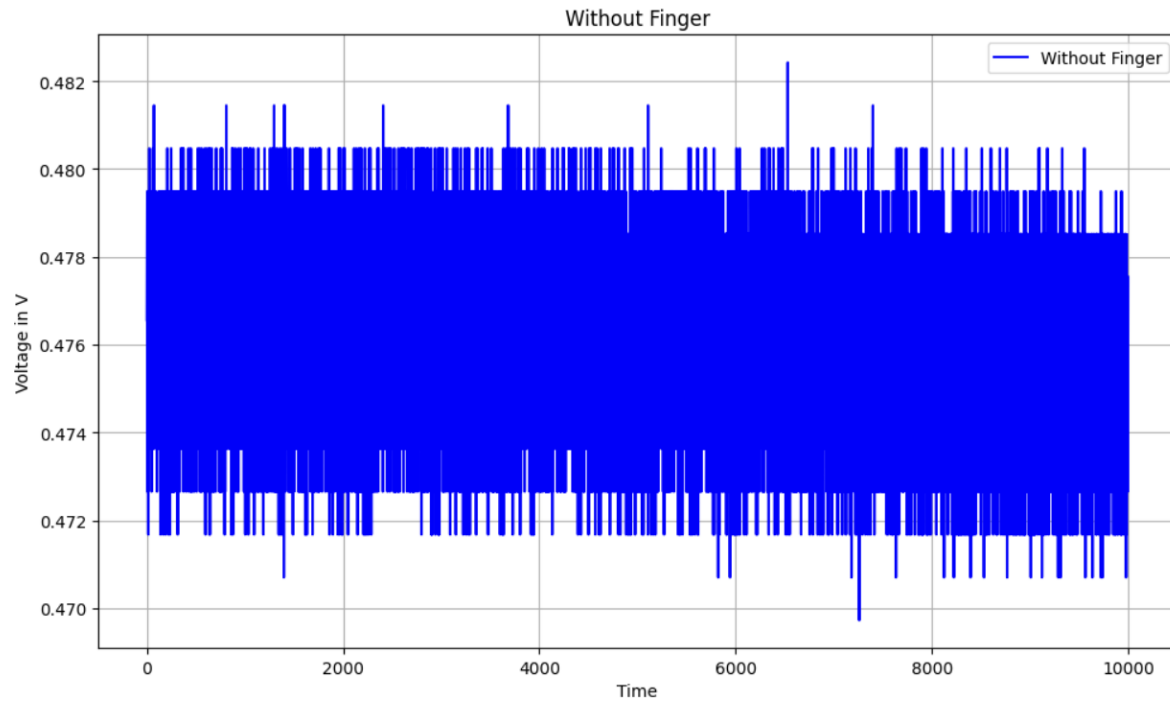

Noise is a random fluctuation of the output of a sensor which is essentially unrelated to the input parameter. Common sources of noise include temperature fluctuations, electromagnetic interference, instability of the bioactive sensitive element or of the electronic circuitry, mechanical vibrations and fluid flow artifacts such as bubbles. Noise can be quantified as the root mean square x_{rms} of a sample ($x_1, x_2, \dots, x_n$) of output signals for a given time period:

$$x_{rms} = \sqrt{\frac{1}{n} \sum_{i=1}^n x_i^2} = \sqrt{\frac{x_1^2 + x_2^2 + \dots + x_n^2}{n}}.$$